
Lecture19:

Common-source amplifier (3)

Sung-Min Hong (smhong@gist.ac.kr)


Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Review of the last lecture

- Why do we consider an active load?
 - A sufficiently large voltage headroom for the DC bias
 - A sufficiently high impedance for the AC current
- When we have R_S ,
 - The voltage gain is reduced.


Current-source load

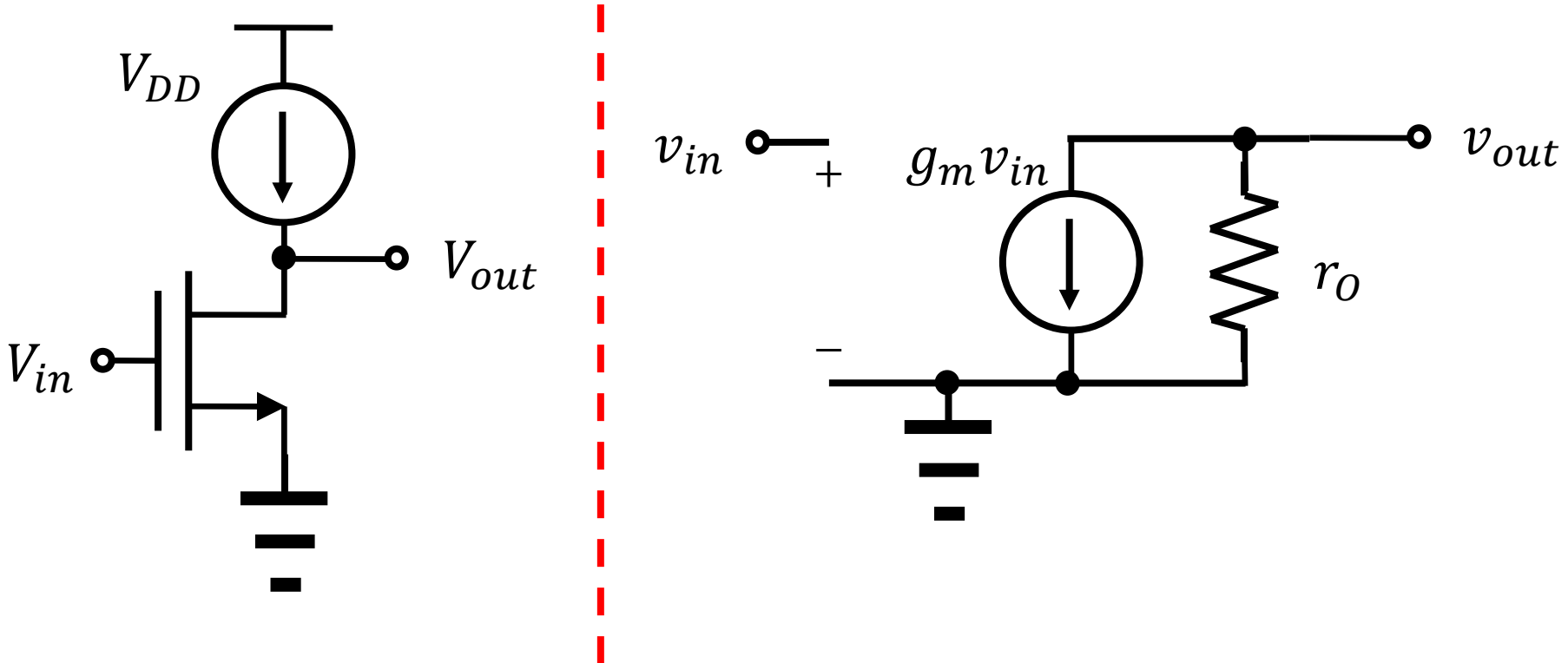- When $R_D \rightarrow \infty$,
 - The gain can be maximized in its absolute value. ($A_v \rightarrow -g_m r_o$)



Biasing of PMOS devices

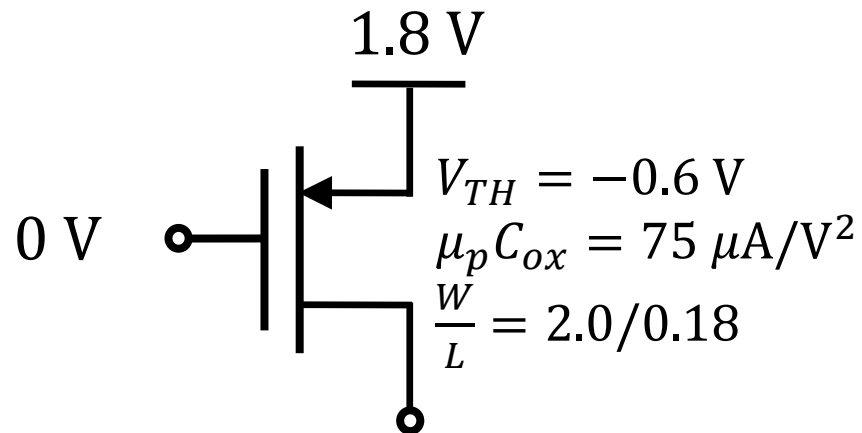- Use a PMOS as a current source
 - The absolute value of the “gate overdrive” is 1.2 V.
 - Of course, when the drain voltage is higher than 0.6 V, it is operated in the triode mode.




Real current-source load

- Use a PMOS as a current source.
 - It is not an ideal current source.


$$v_{out} = -g_{m1}(r_{O1}||r_{O2})v_{in}$$

$$A_v = -g_{m1}(r_{O1}||r_{O2})$$

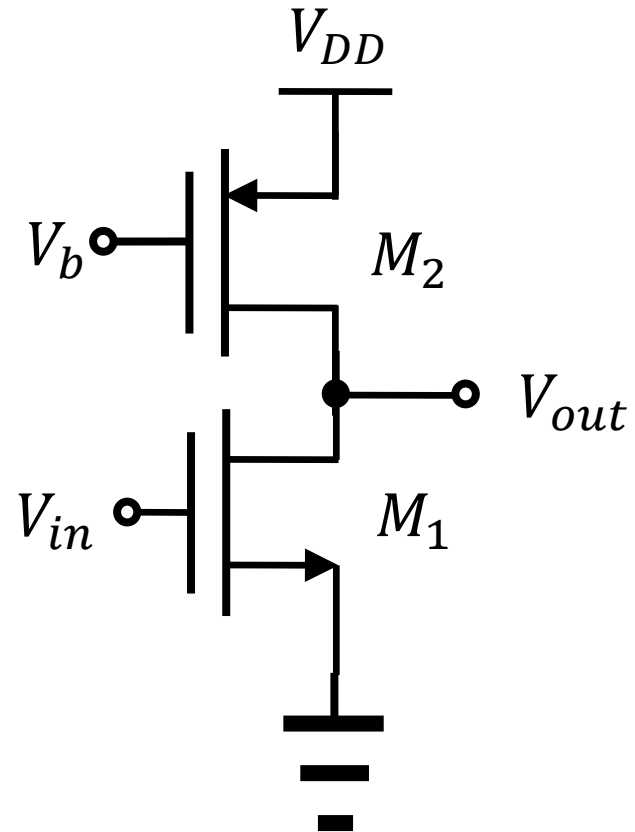

Self-biasing

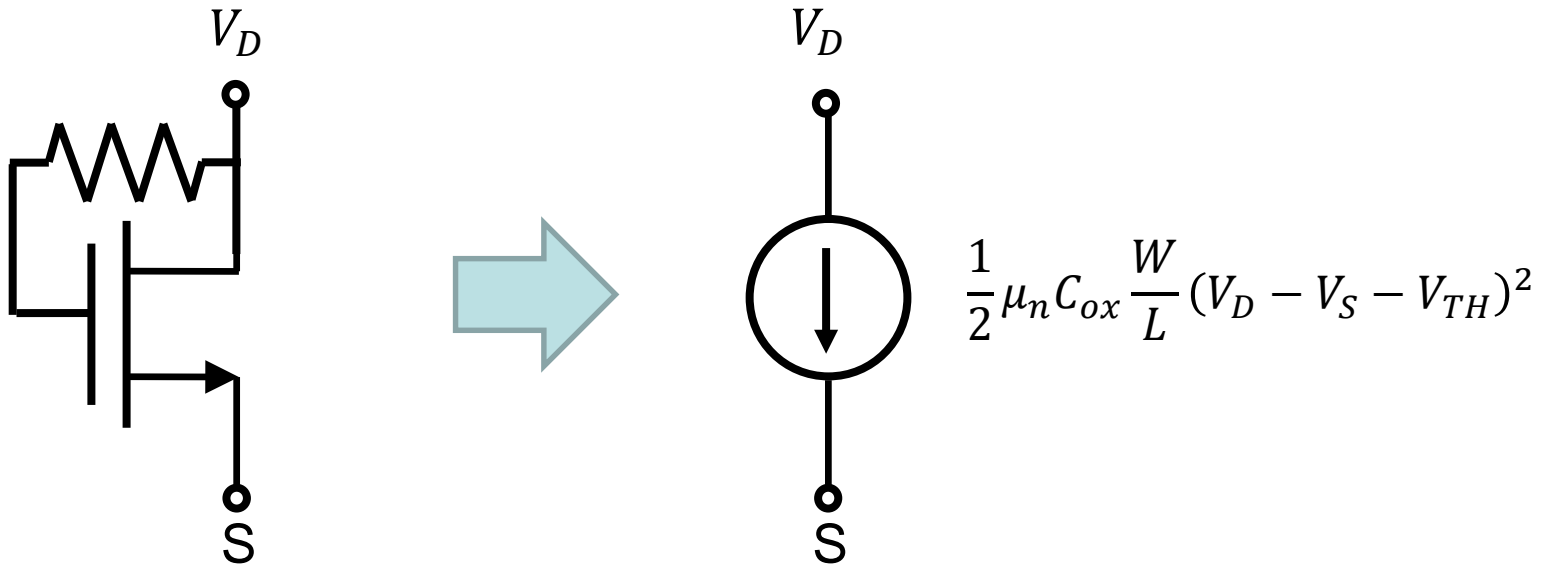- Already covered in Razavi Example 6.13.
 - Always in the saturation region.




Gate and drain are tied.

Diode-connected load

- Use a diode-connected load.
 - It is not an ideal current source.

$$v_{out} = -g_{m1} \left(r_{O1} \parallel \frac{1}{g_{m2}} \parallel r_{O2} \right) v_{in}$$
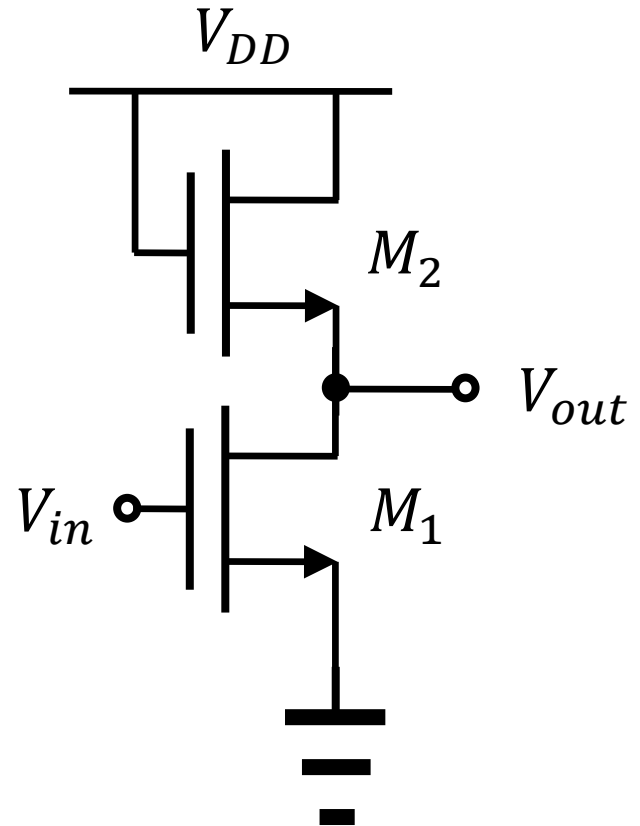
$$A_v = -g_{m1} \left(r_{O1} \parallel \frac{1}{g_{m2}} \parallel r_{O2} \right)$$




Input/output impedances

- When calculating the impedance, the voltage sources at other terminals are neglected.
- Input and output impedances


$$R_{in} = \infty$$

$$R_{out} = R_D || r_o$$

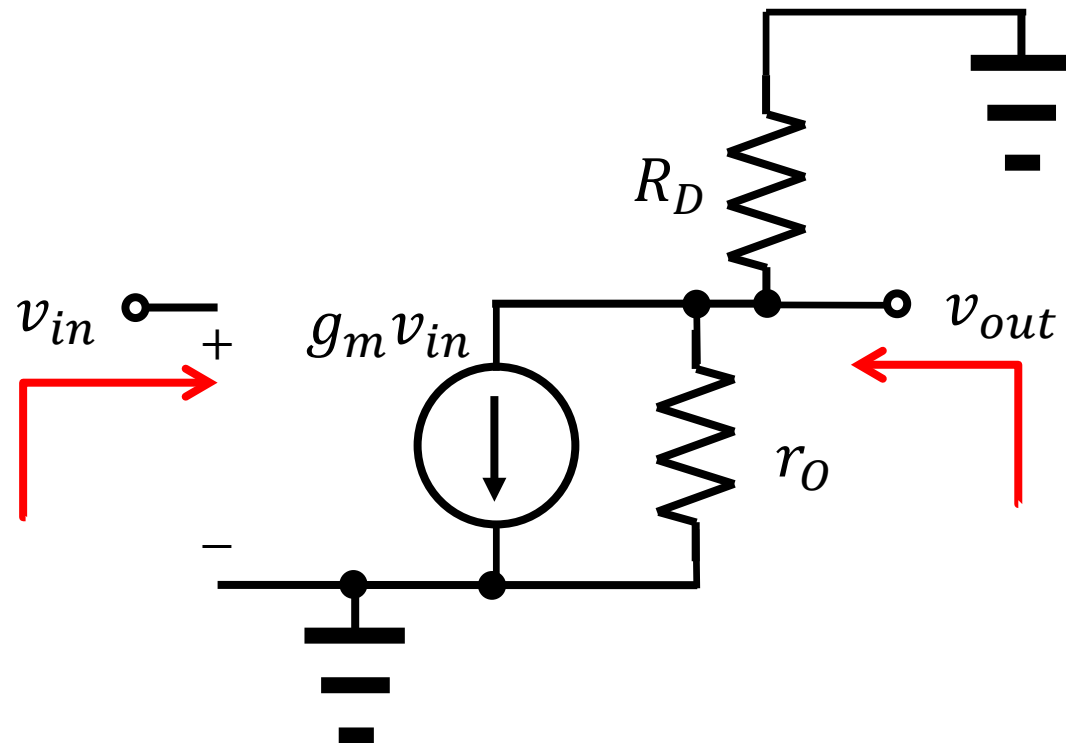

Source degeneration

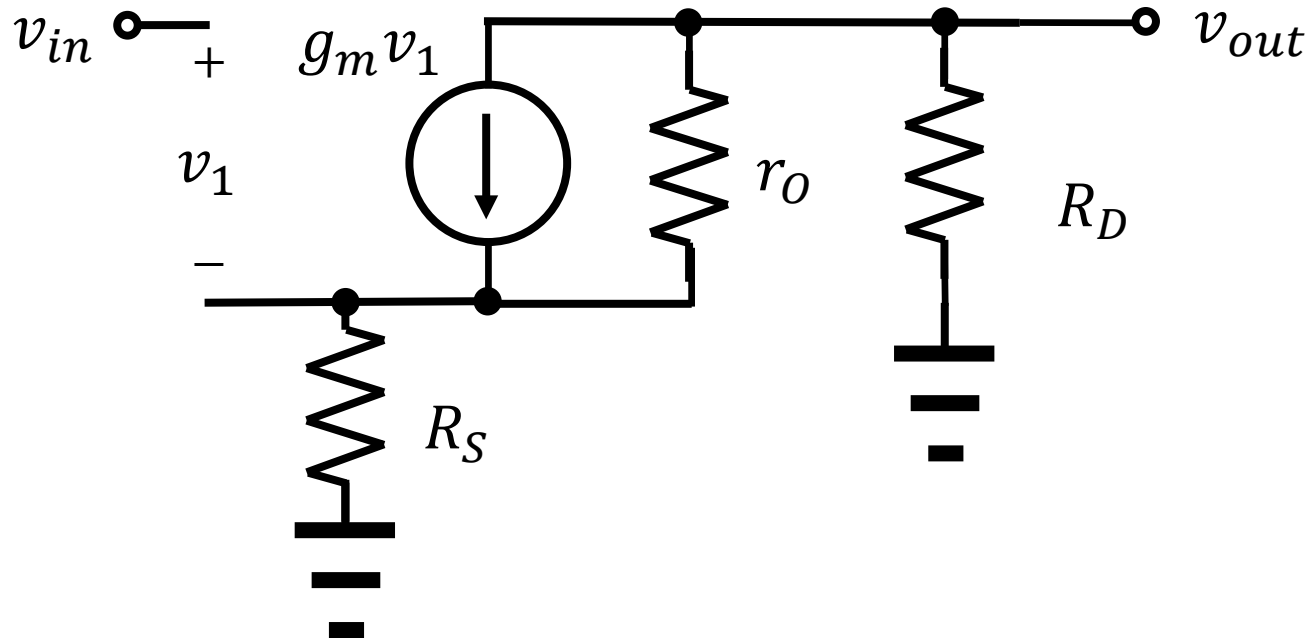- Consider a case with a source resistor, R_S .
 - Calculate the gain and the output impedance.




Razavi, example 17.8

- Biasing

- What is the gate voltage?
- Condition for saturation mode?
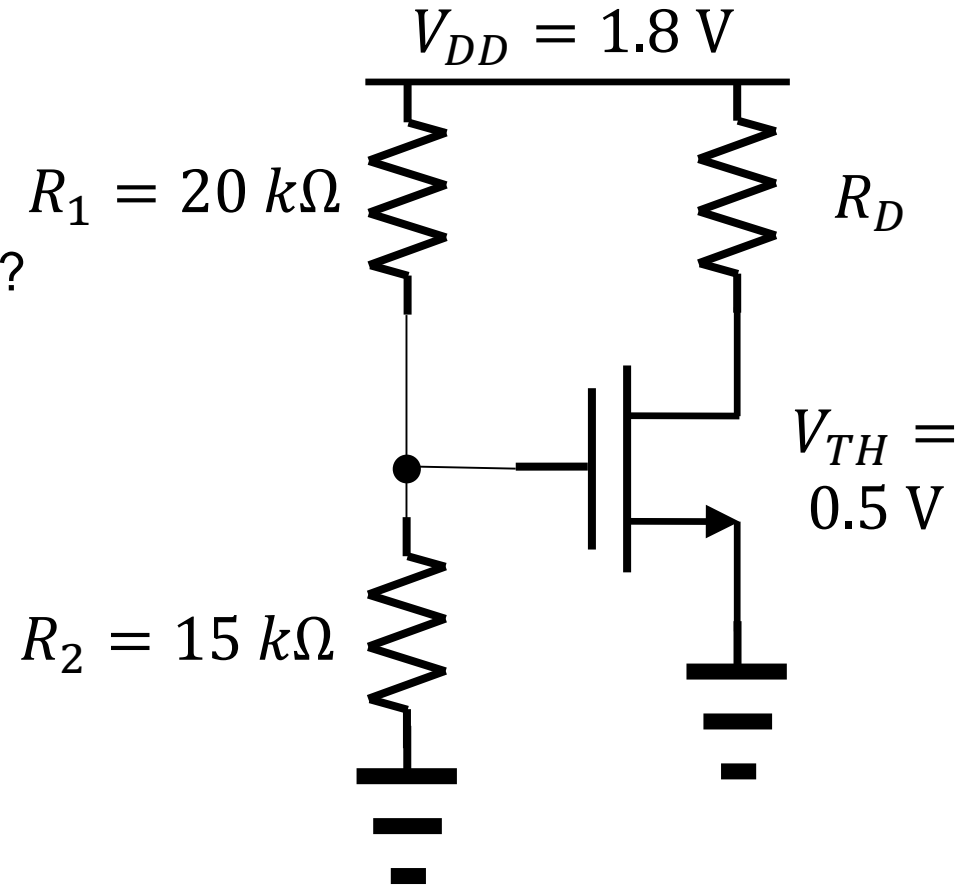
$$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$
$$W/L = 5/0.18$$



Razavi, example 17.13

- Calculate the drain current. (BTW, where is the drain?)

