
Lecture20: Other amplifiers

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Review of the last lecture


- Active loads
 - Ideal current source
 - PMOS
 - NMOS
- Concept of input impedance
 - Why do we need it?

Input/output impedances

- When calculating the impedance, the voltage sources at other terminals are neglected.
- Input and output impedances


$$R_{in} = \infty$$

$$R_{out} = R_D || r_o$$

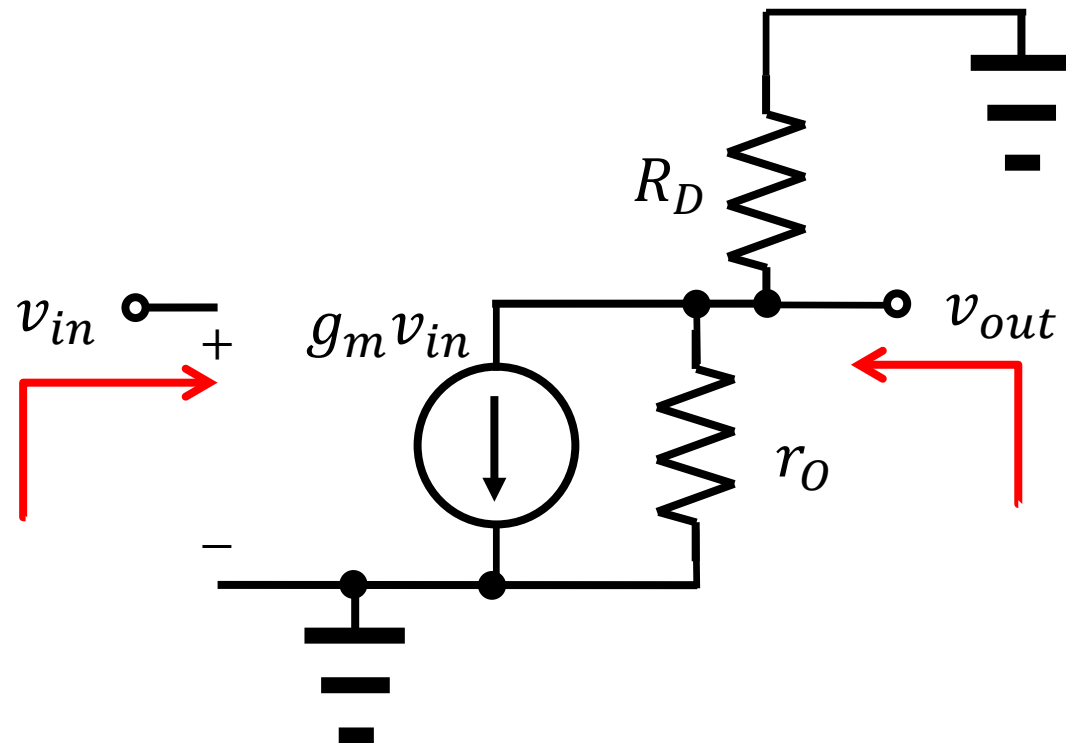

Source degeneration

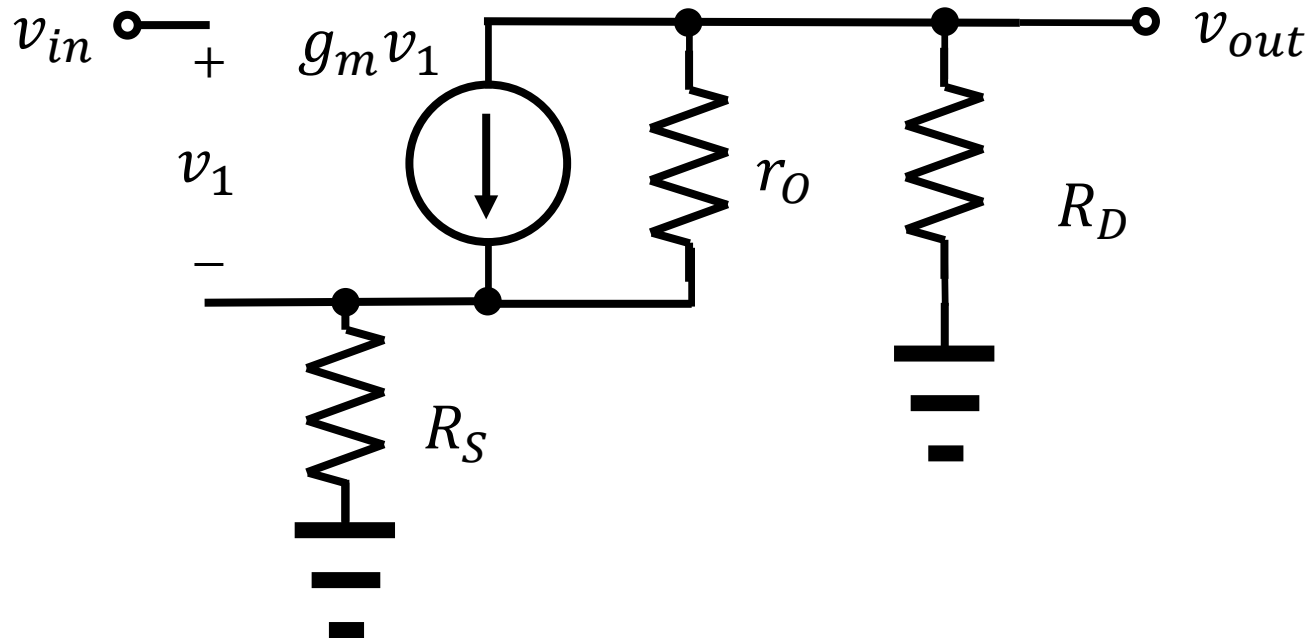- Consider a case with a source resistor, R_S .
 - Calculate the gain and the output impedance.




Razavi, example 17.8

- Biasing


- What is the gate voltage?
- Condition for saturation mode?
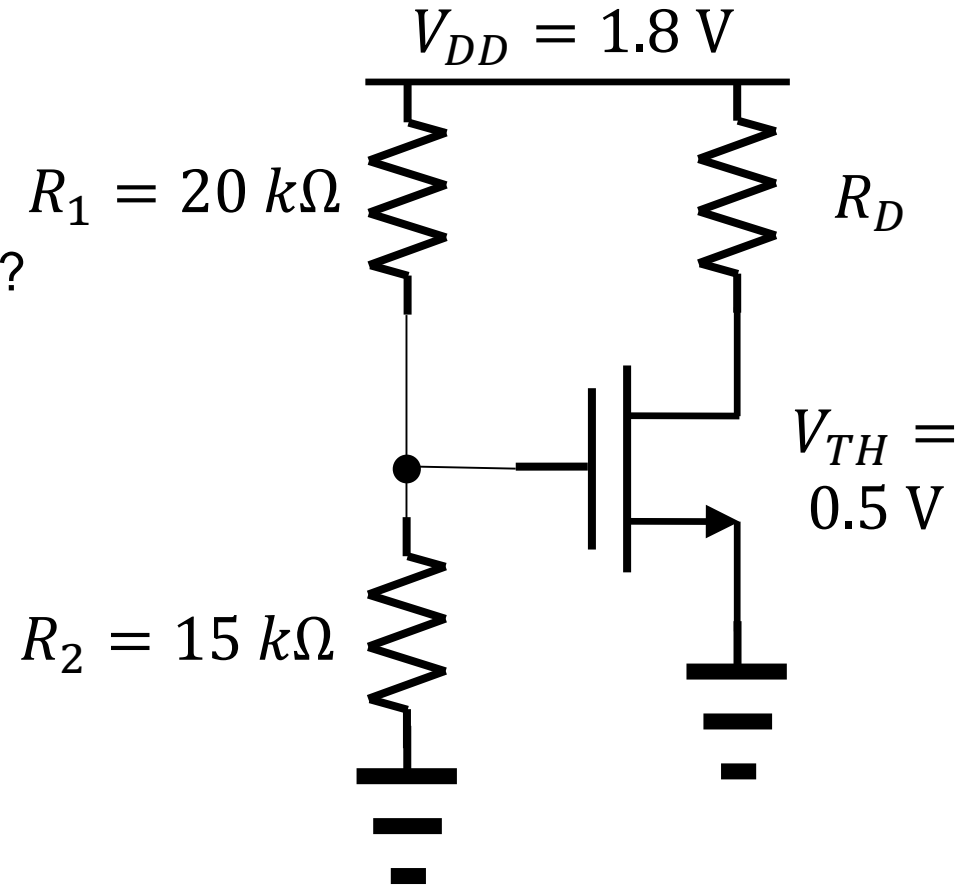
$$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$
$$W/L = 5/0.18$$



Razavi, example 17.13

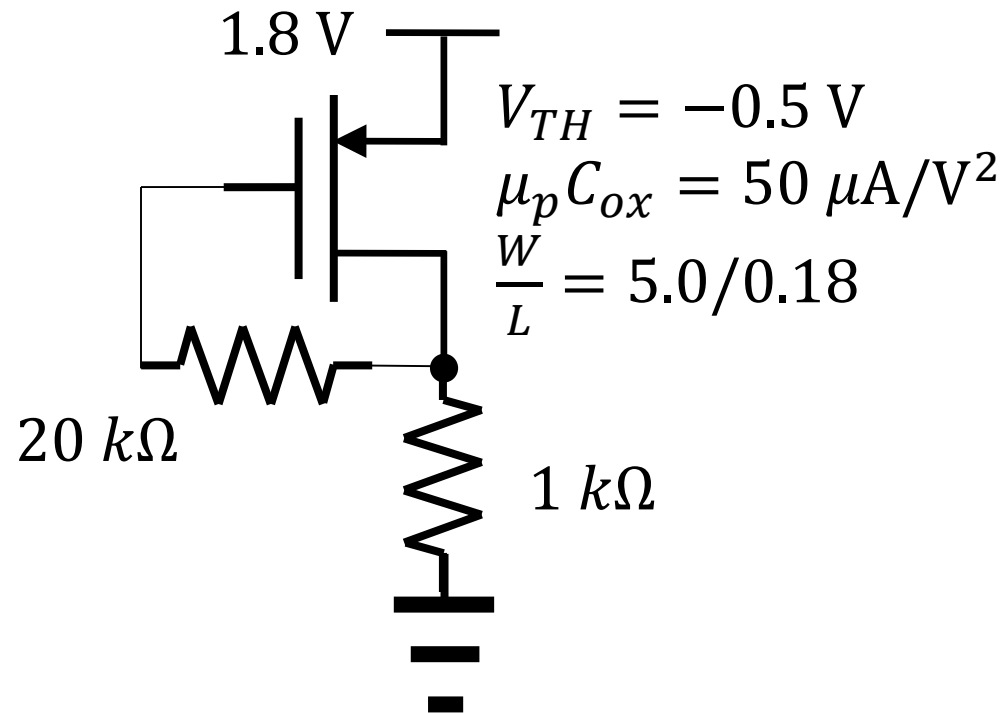- Calculate the drain current. (BTW, where is the drain?)




Configurations

- Three terminals of the MOSFET
 - The common terminal, the input terminal, and the output terminal

| Source | Gate | Drain | Remark |
|--------|--------|--------|---------------------|
| Common | Input | Output | Common-source amp. |
| Common | Output | Input | X |
| Input | Common | Output | It will be covered. |
| Output | Common | Input | X |
| Input | Output | Common | X |
| Output | Input | Common | It will be covered. |


Common-gate amplifier

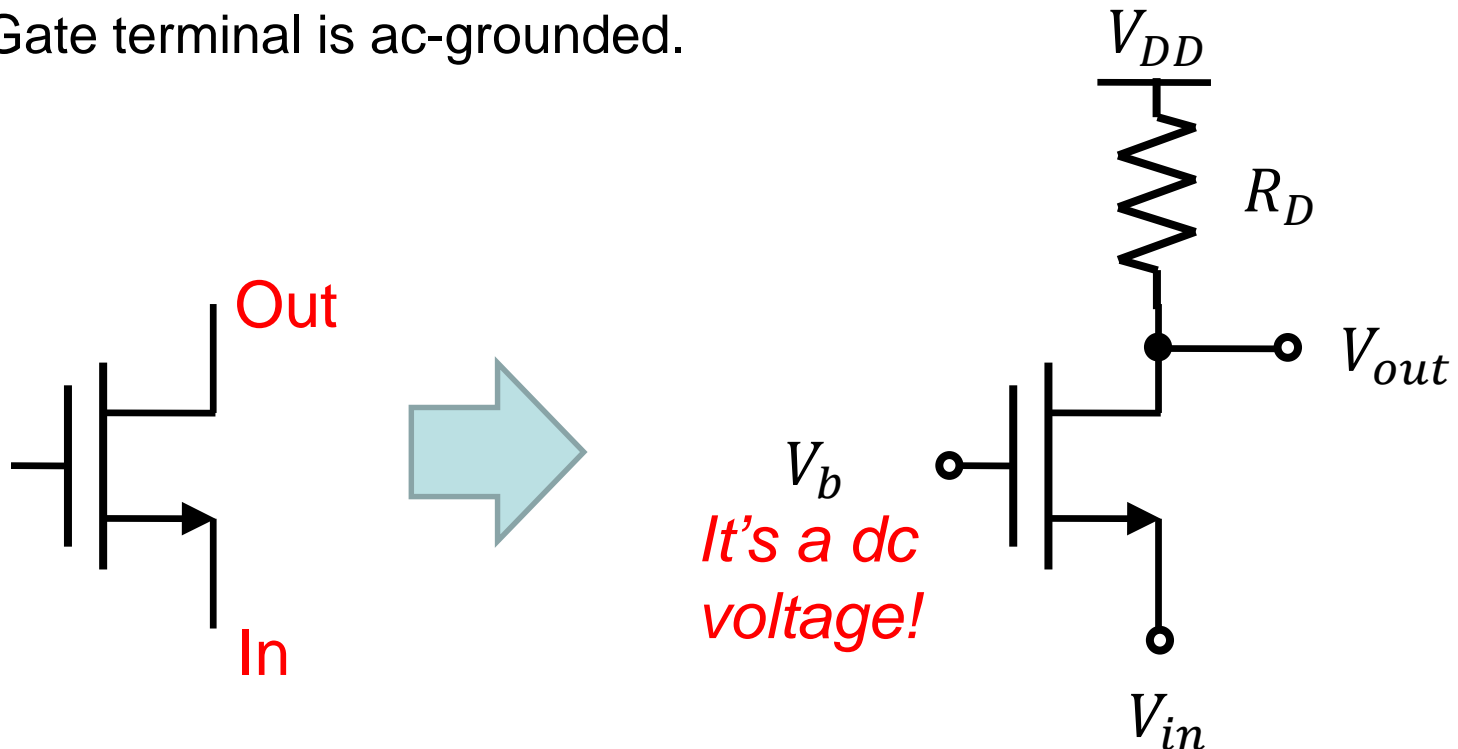- Why do we study other amplification topologies?
 - Different circuit properties
- Common-gate amplifier
 - Gate terminal is ac-grounded.



Small-signal model

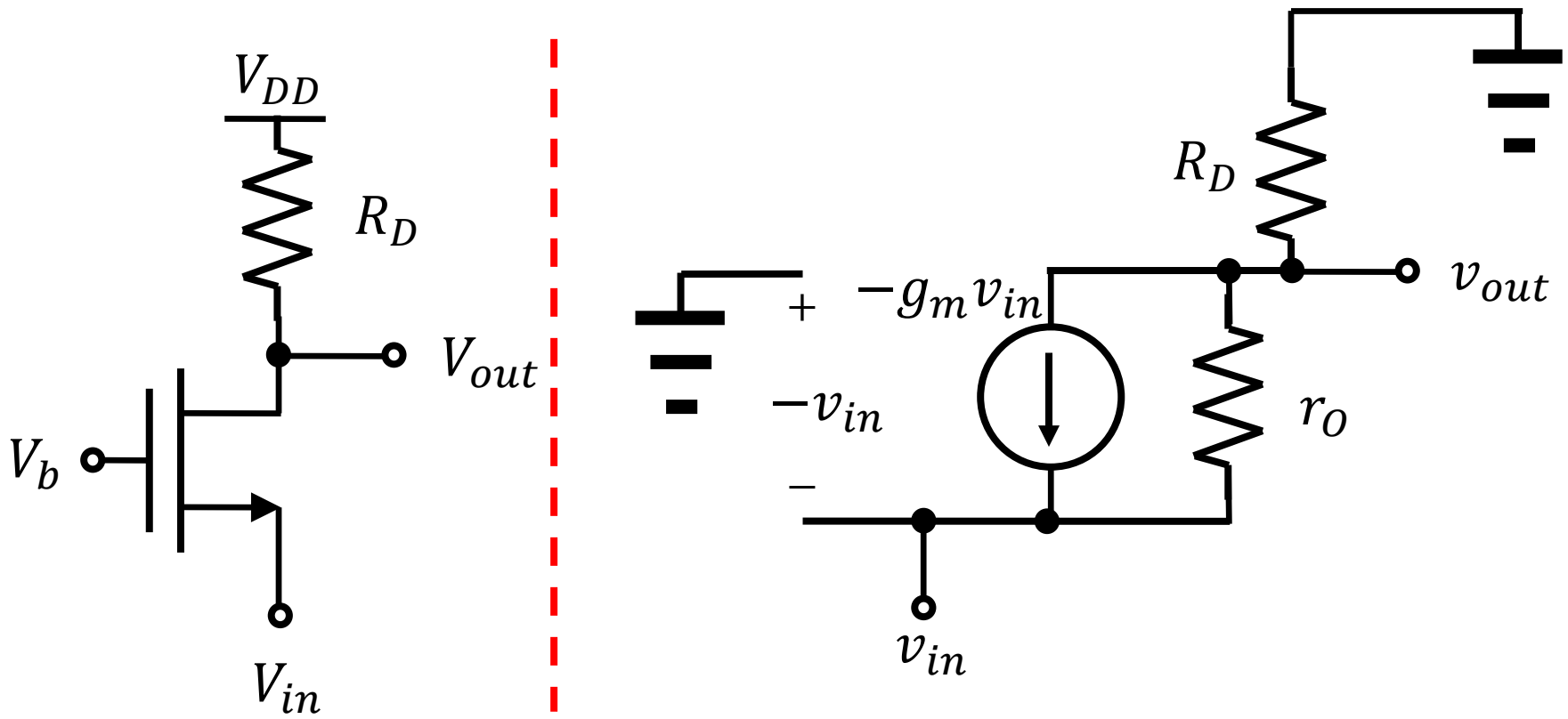- Let's draw the small-signal model together!



Gain & input impedance (1/2)

- Neglect the output resistance, r_o .


- Voltage gain

$$A_v = +g_m R_D$$

- Input impedance

$$R_{in} = \frac{1}{g_m}$$

It's small!

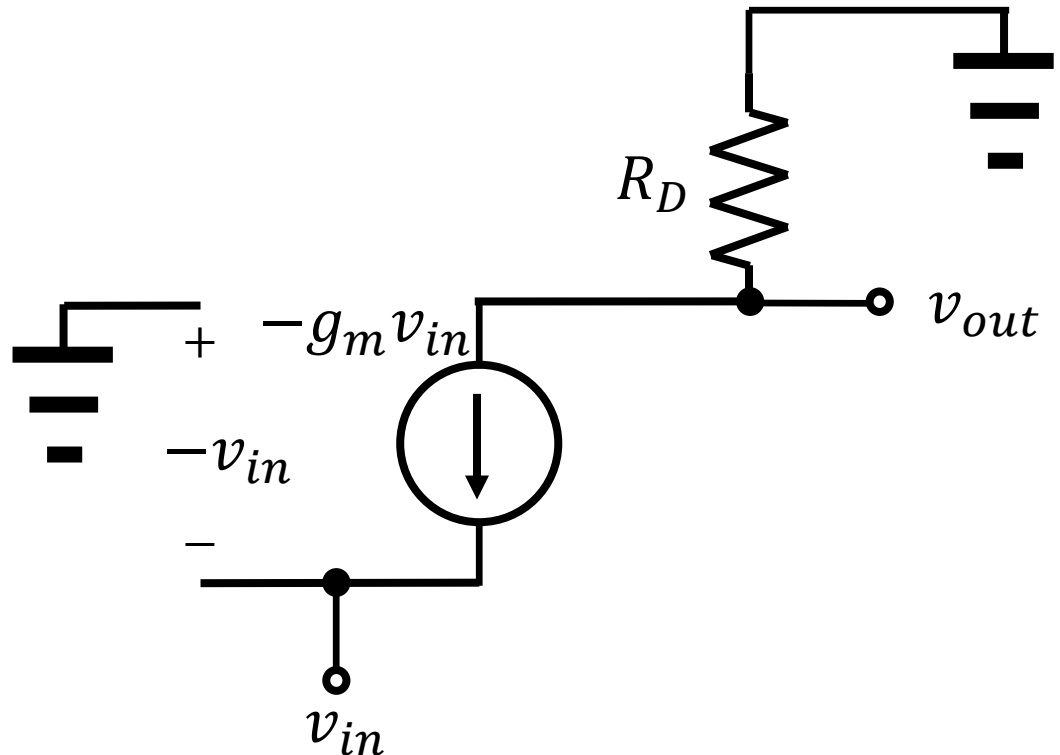

Gain & input impedance (2/2)

- Consider the output resistance, r_o .


- Voltage gain

$$A_v = + \left(g_m + \frac{1}{r_o} \right) (R_D || r_o)$$

- Input impedance


$$R_{in} = \frac{r_o + R_D}{g_m r_o + 1}$$

It's small!

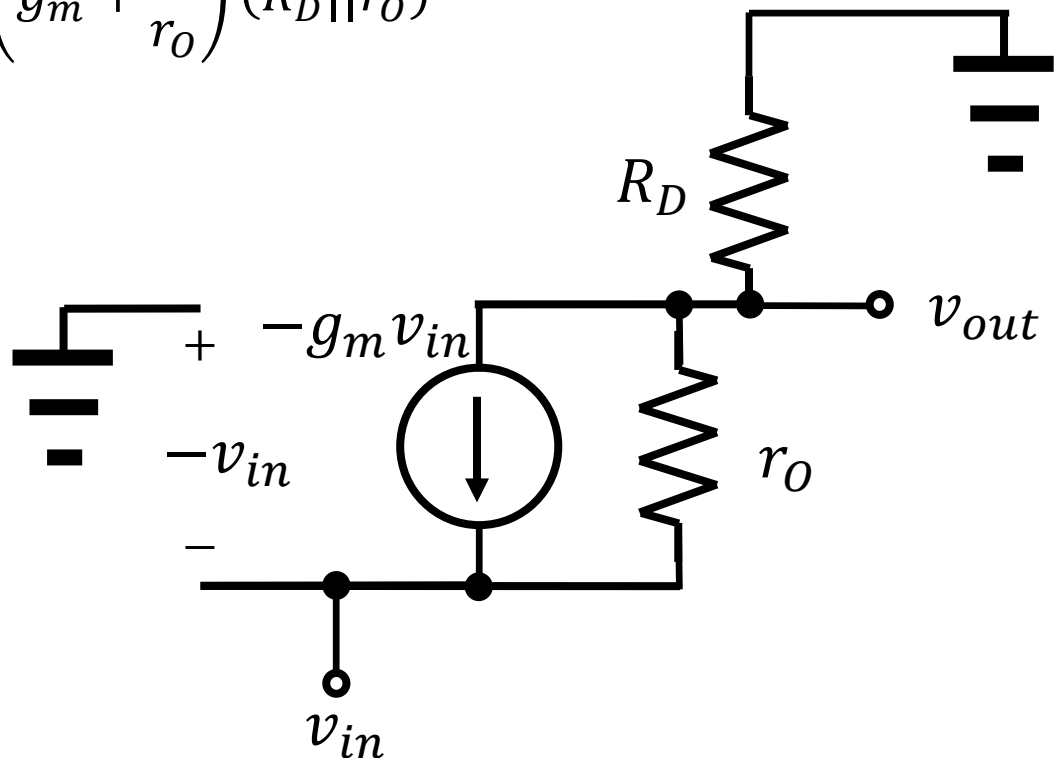


Output impedance

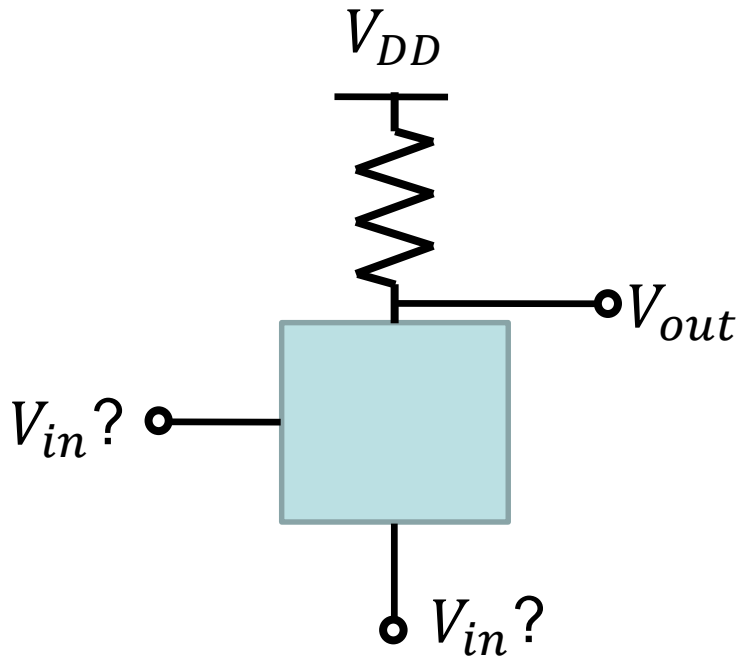- Without a finite source resistance, $R_{out} = r_o \parallel R_D$






Generic form of CS and CG stages

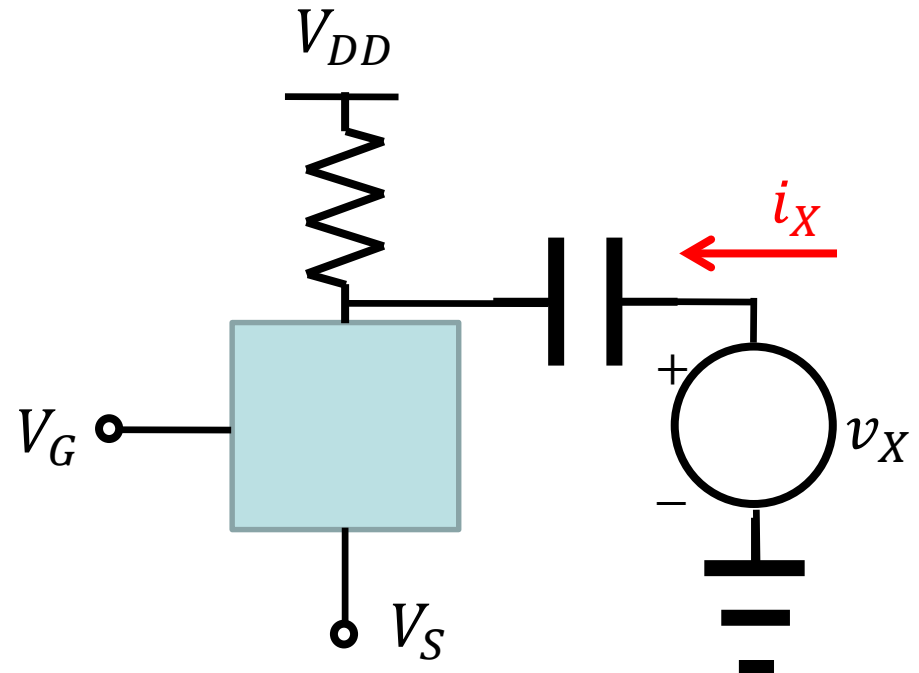

Setting for calculating R_{out}

Source follower

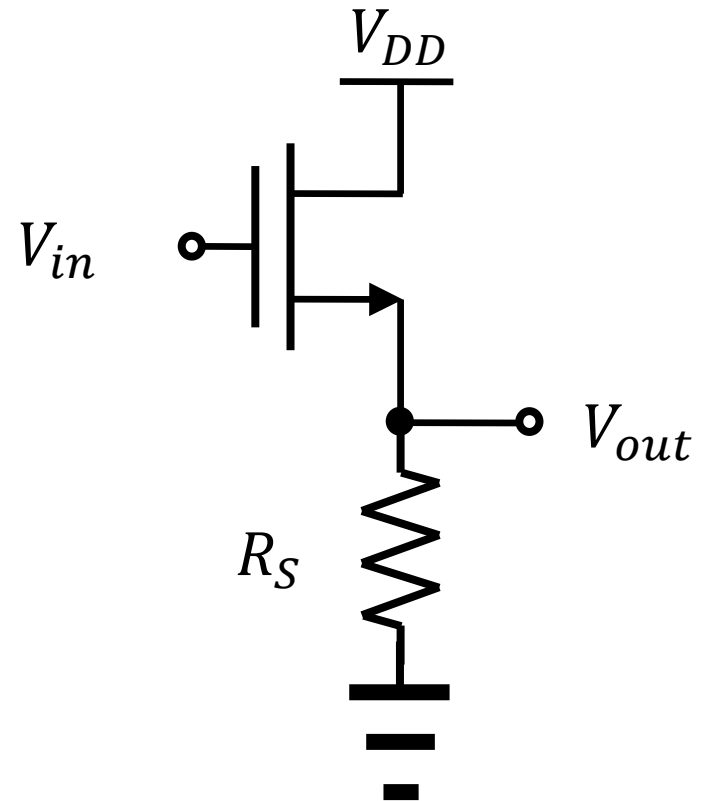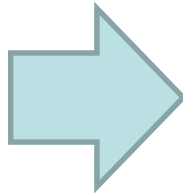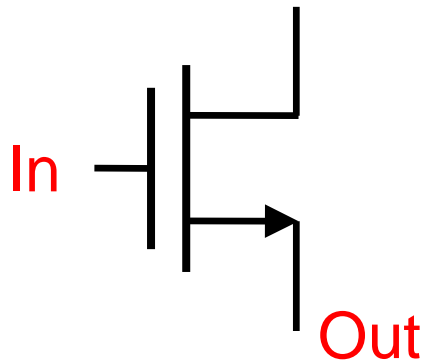
- Also called the “common-drain” stage
 - The drain is ac grounded.
- Wait a minute!
 - Is it a real amplifier?



Its core

- Gain is less than 1?? (Neglecting r_o)

$$A_v = + \frac{g_m R_S}{1 + g_m R_S}$$

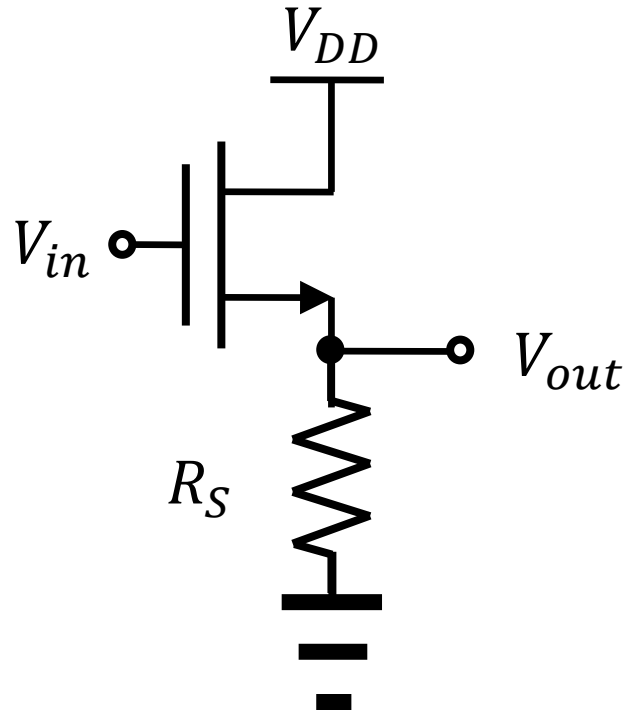


You should be able to draw the small-signal model.

Useless?

- Calculate the input and output impedances.
 - Since the gate is the input terminal, the input impedance is very high at low frequencies.
 - How about the output impedance?


$$R_{out} = \frac{1}{g_m} || r_o || R_S$$

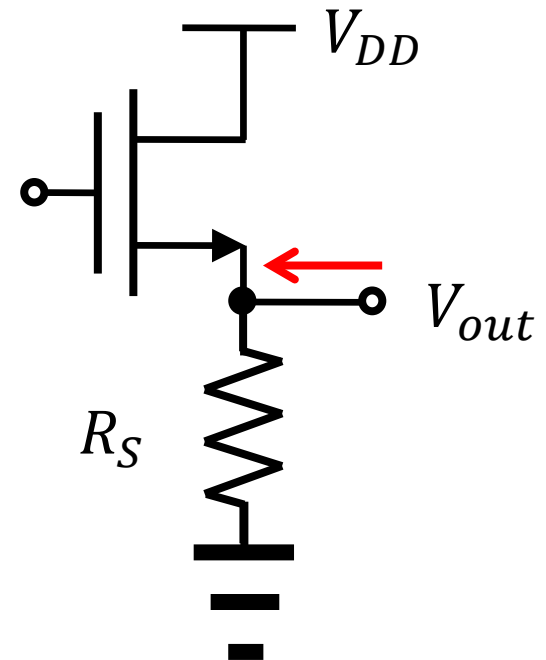- It is relatively low.
- High input imp., low output imp.
 - They can serve as good “buffers.”




Razavi, example 17.36

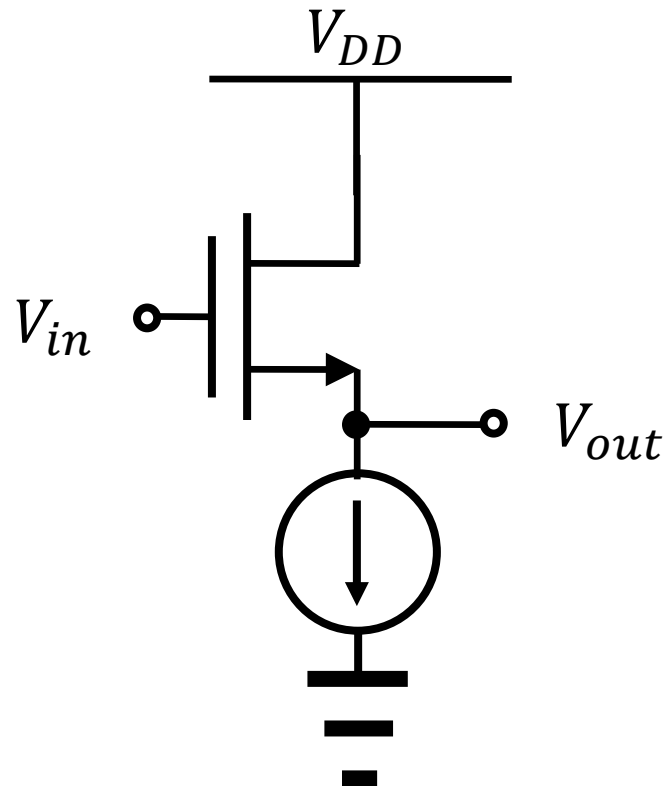- In integrated circuits, the follower is typically realized as shown below. Determine the voltage gain if the current source is ideal. Neglect the channel-length modulation.



Razavi, example 17.37

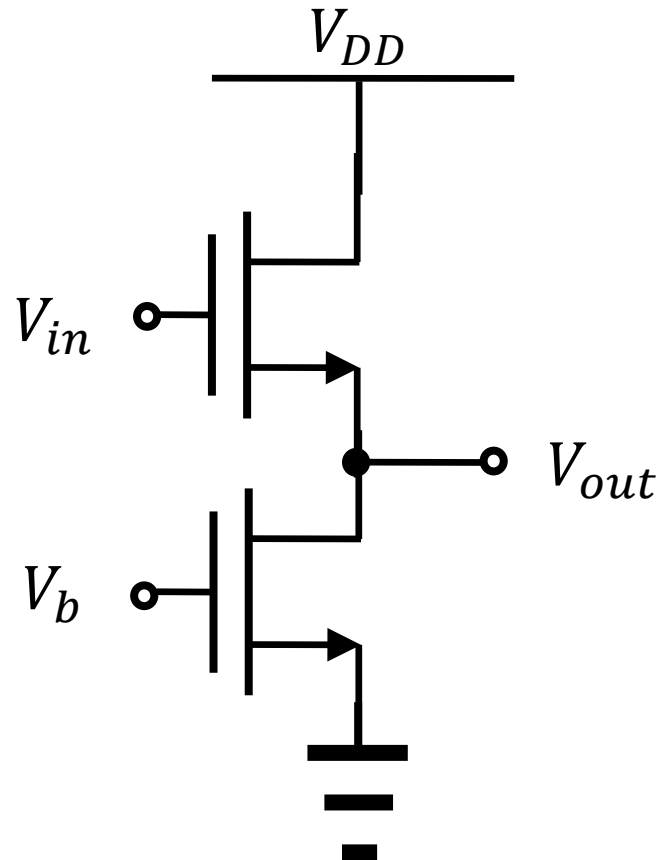- A source follower is realized as shown below. Calculate the voltage gain of the circuit.



Razavi, example 17.39

- Design the source follower.
 - Determine W/L and R_S .
 - The DC drain current is 1 mA.
 - The voltage gain is 0.8.

