
Lecture6: Diode

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

A circuit with two resistors

- Analyze the following circuit.
 - Two equations from the KCL (Let's avoid nested subscripts.)


$$I_{VA} + I_{R2} = 0$$
$$-I_{R2} + I_{R1} = 0$$

- Three equations from elements

$$V_{in} = V_A$$
$$I_{R2} = \frac{V_{in} - V_{out}}{R_2}$$

$$I_{R1} = \frac{V_{out}}{R_1}$$

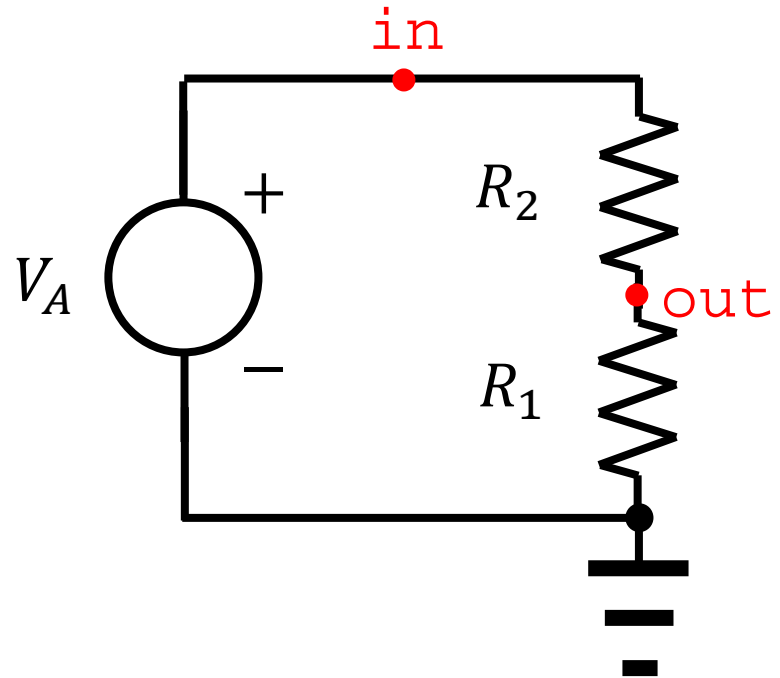- We can solve it easily.
 - A set of linear equations



A circuit with a diode

- Then, analyze the following circuit.

- Two equations from the KCL

$$I_{V_A} + I_{D1} = 0$$

$$-I_{D1} + I_{R1} = 0$$

- Three equations from elements


$$V_{in} = V_A$$

$$I_{D1} = I_s \left(\exp \left(\frac{V_{in} - V_{out}}{V_T} \right) - 1 \right)$$

$$I_{R1} = \frac{V_{out}}{R_1}$$

- We CANNOT solve it easily.

- A set of nonlinear equations

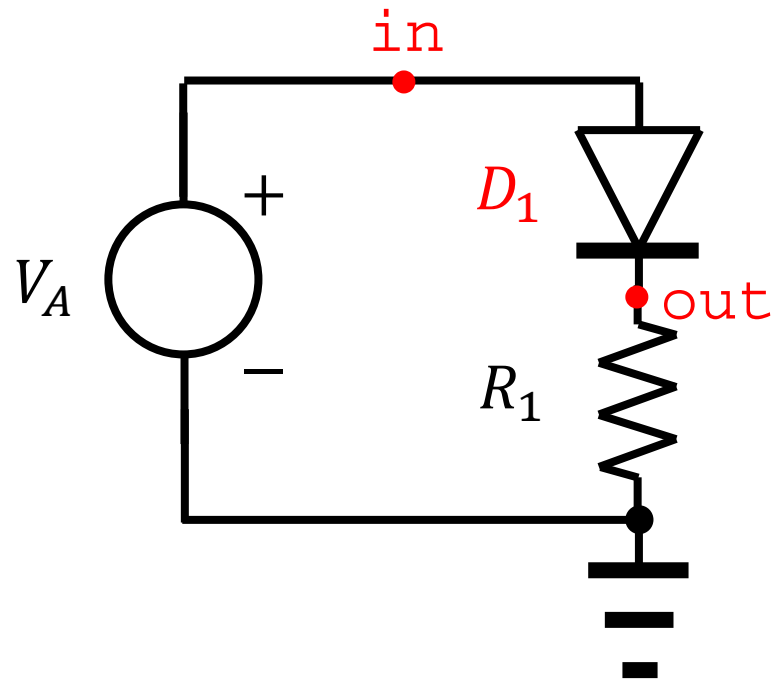

General solution

- Solve the set of equations.

- After simple manipulation, it is easily found that

$$r(V_{out}) = -I_S \left(\exp \left(\frac{V_A - V_{out}}{V_T} \right) - 1 \right) + \frac{V_{out}}{R_1} = 0$$

- A nonlinear equation for V_{out} is obtained.

- An example inspired by Razavi, Example 2.21

- In this example,

$$I_S = 10^{-16} \text{ A}$$

$$R_1 = 1 \text{ k}\Omega$$

$$V_A = 1 \text{ V}$$

- Assume 300 K.
 - How can we solve it?

Iterative method

- Trial-and-error

- Try $V_{out} = 1$ V. (Of course, it is not a solution.)
- Then, we have

$$r(V_{out} = 1 \text{ V}) = \frac{1 \text{ V}}{1 \text{ k}\Omega} = 1 \text{ mA} \neq 0$$


- Okay, (as expected) it is not a solution. How about $V_{out} = 0.9$ V?
- Then, we have

$$r(V_{out} = 0.9 \text{ V}) = -10^{-16} \text{ A} \times \left(\exp\left(\frac{0.1 \text{ V}}{V_T}\right) - 1 \right) + \frac{0.9 \text{ V}}{1 \text{ k}\Omega} = 0.9 \text{ mA} \neq 0$$

- How about $V_{out} = 0.8$ V?
- How about $V_{out} = 0.7$ V?
- How about $V_{out} = 0.6$ V?
- How about $V_{out} = 0.5$ V?
- Repeat it until you get the solution...


Visualization of $r(V_{out})$

- Nonlinear function

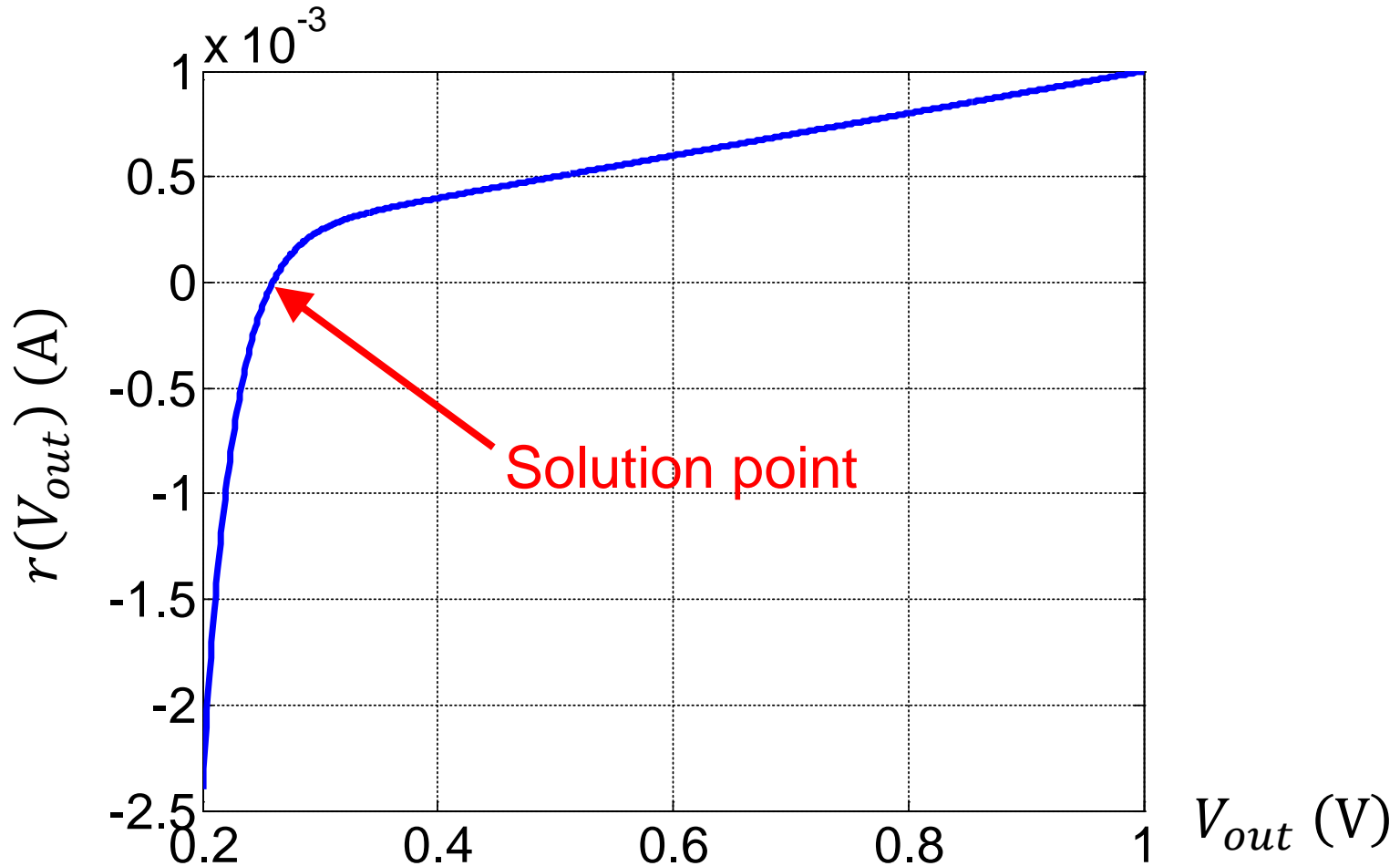


Diode I-V curves

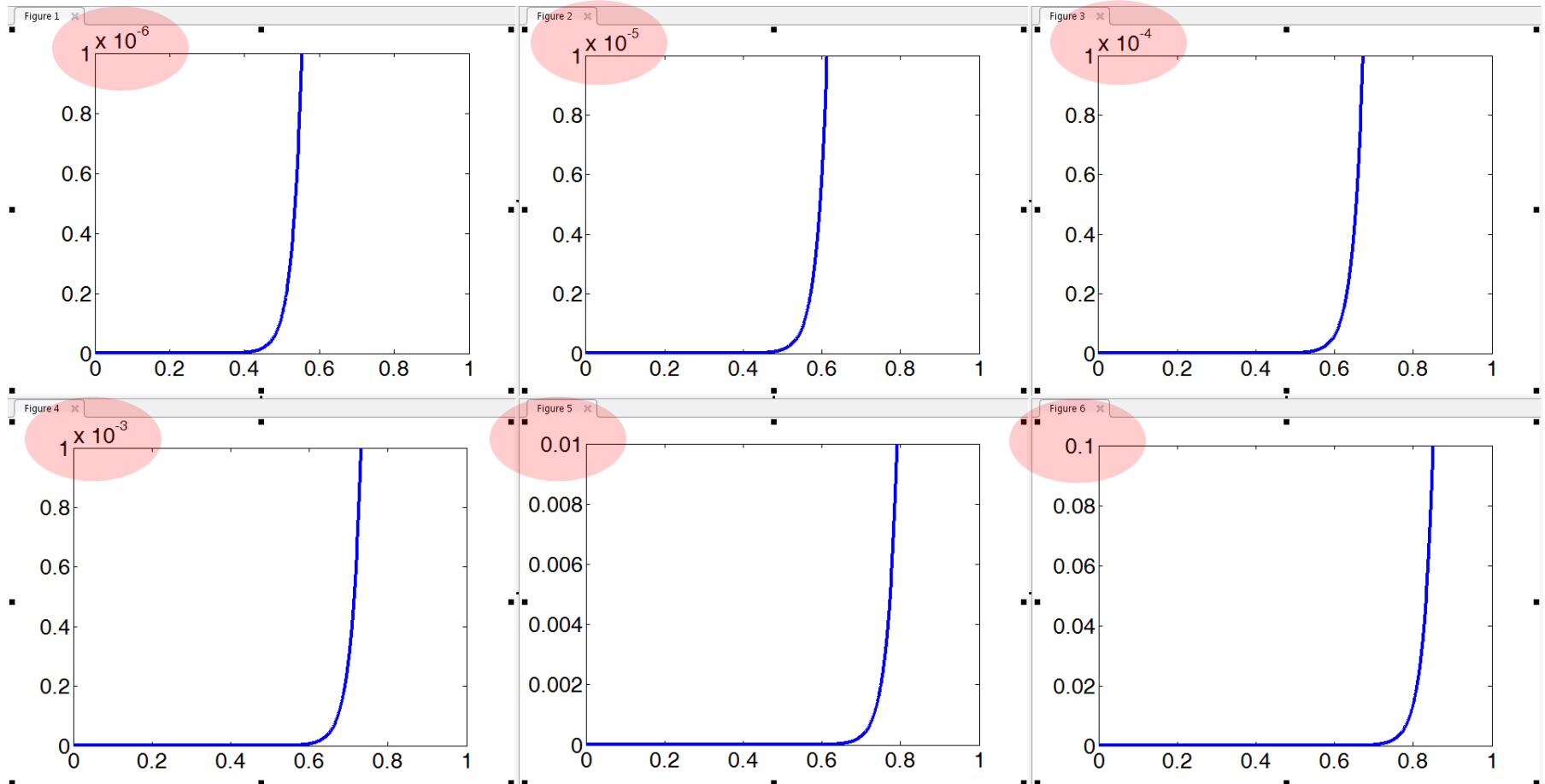- A diode with $I_S = 5 \times 10^{-16} \text{ A}$ (Only different y scales)




Important observation

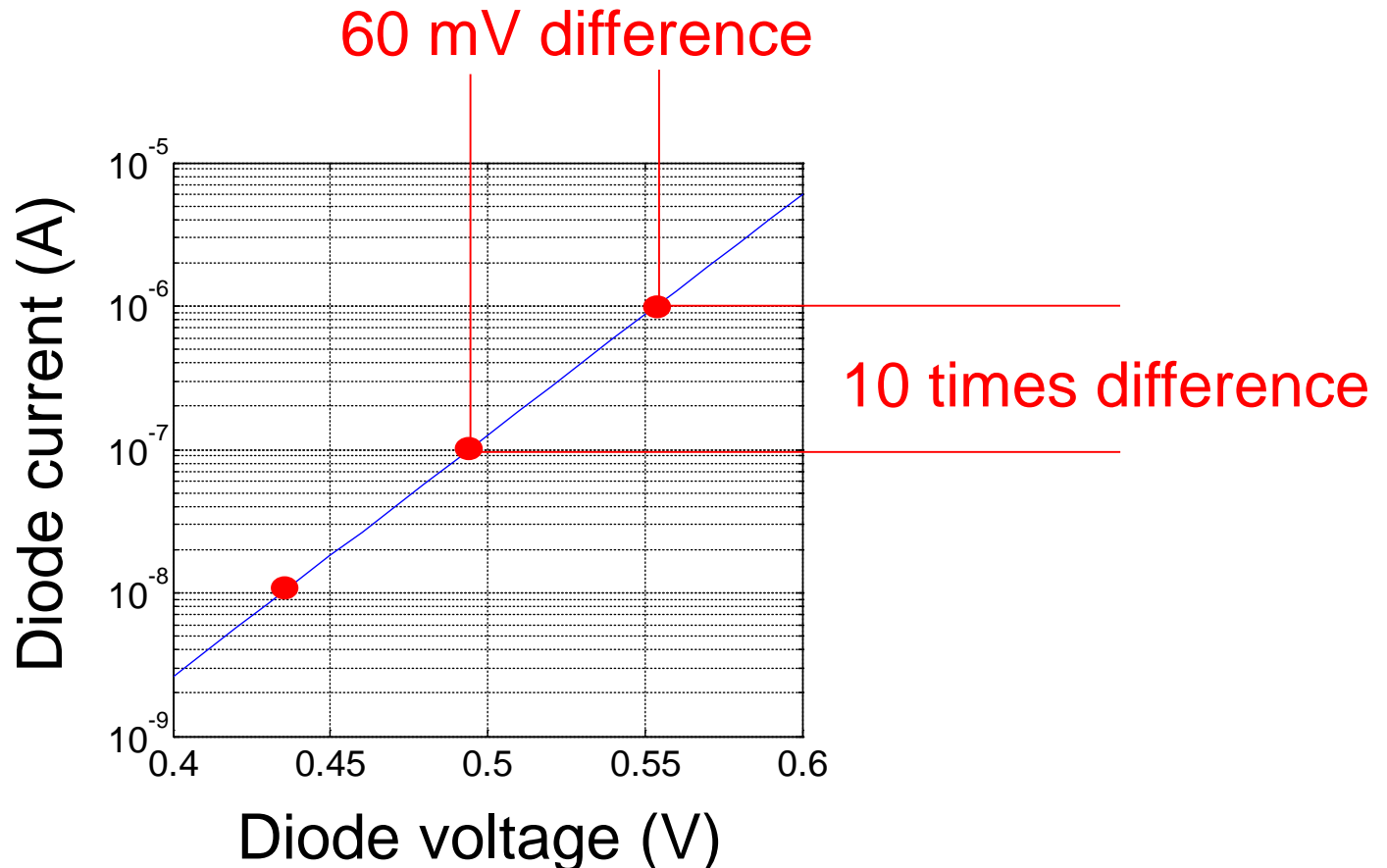- In order to obtain 10x larger current,
 - We must apply only 60 mV additionally. (300K)




Constant-voltage model

- Two phases

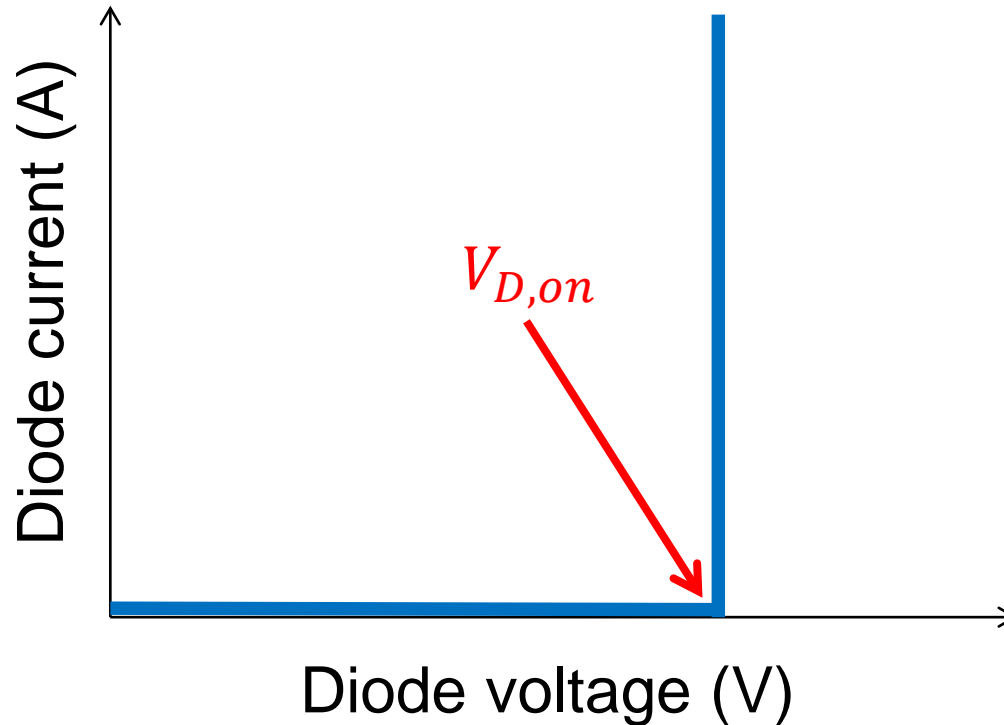

Confused by abrupt increase?

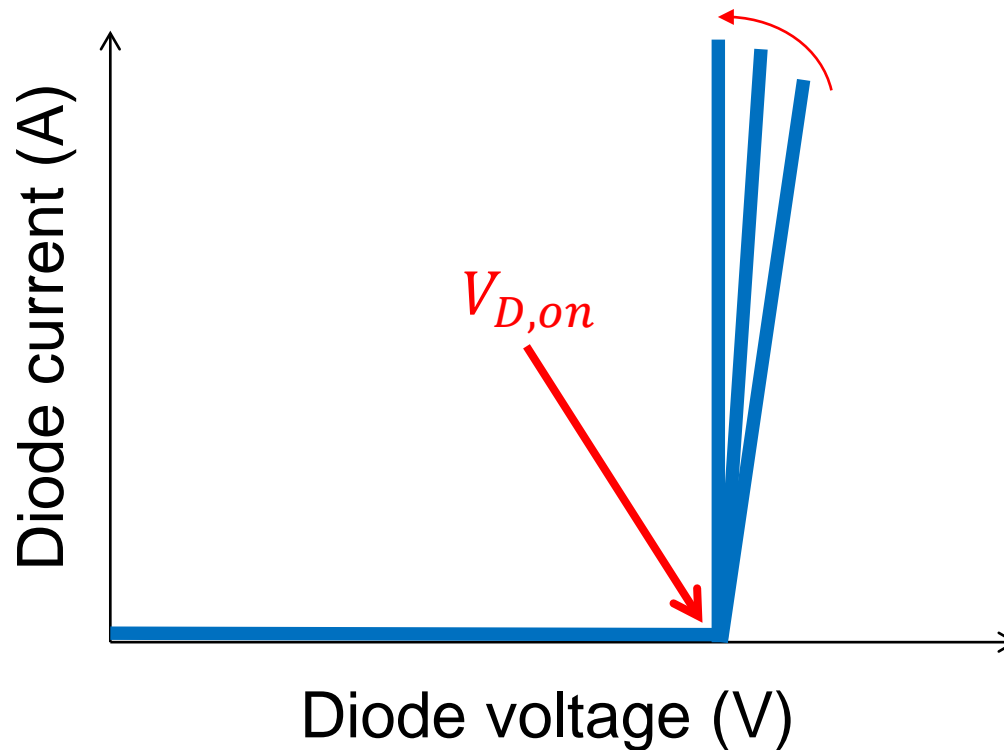- The vertical line should be interpreted as
 - A limiting case of a very steep slope



Revisiting our example

- Our previous example


- In this example,

$$I_S = 10^{-16} \text{ A}$$

$$R_1 = 1 \text{ k}\Omega$$


$$V_A = 1 \text{ V}$$

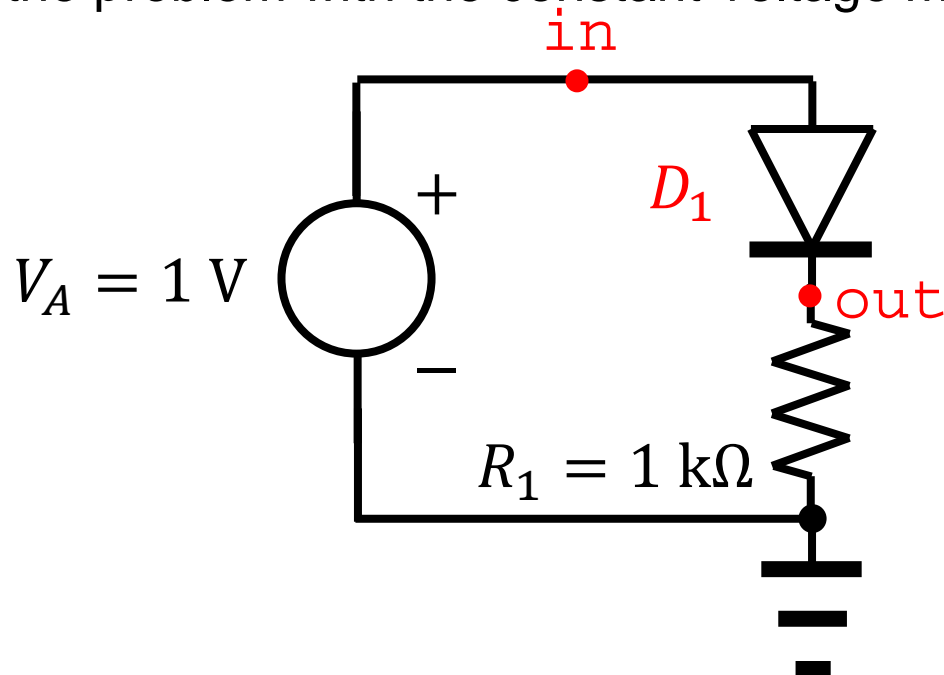- Solve the problem with the constant-voltage model.




Turned off?

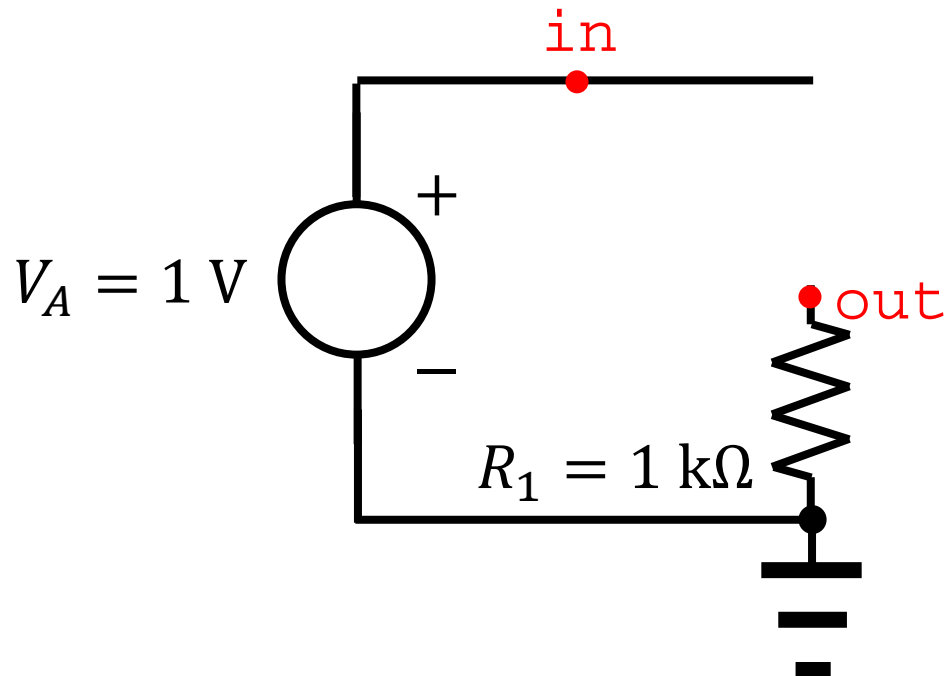- Assume that the diode is turned off.
 - Then, the diode does not conduct a current.
 - Calculate V_{out} . Obviously, it must be 0 V.
 - However, it means that 1 V is applied to the diode. Since 1 V is certainly larger than $V_{D,on}$, our assumption does not hold.



Turned on?

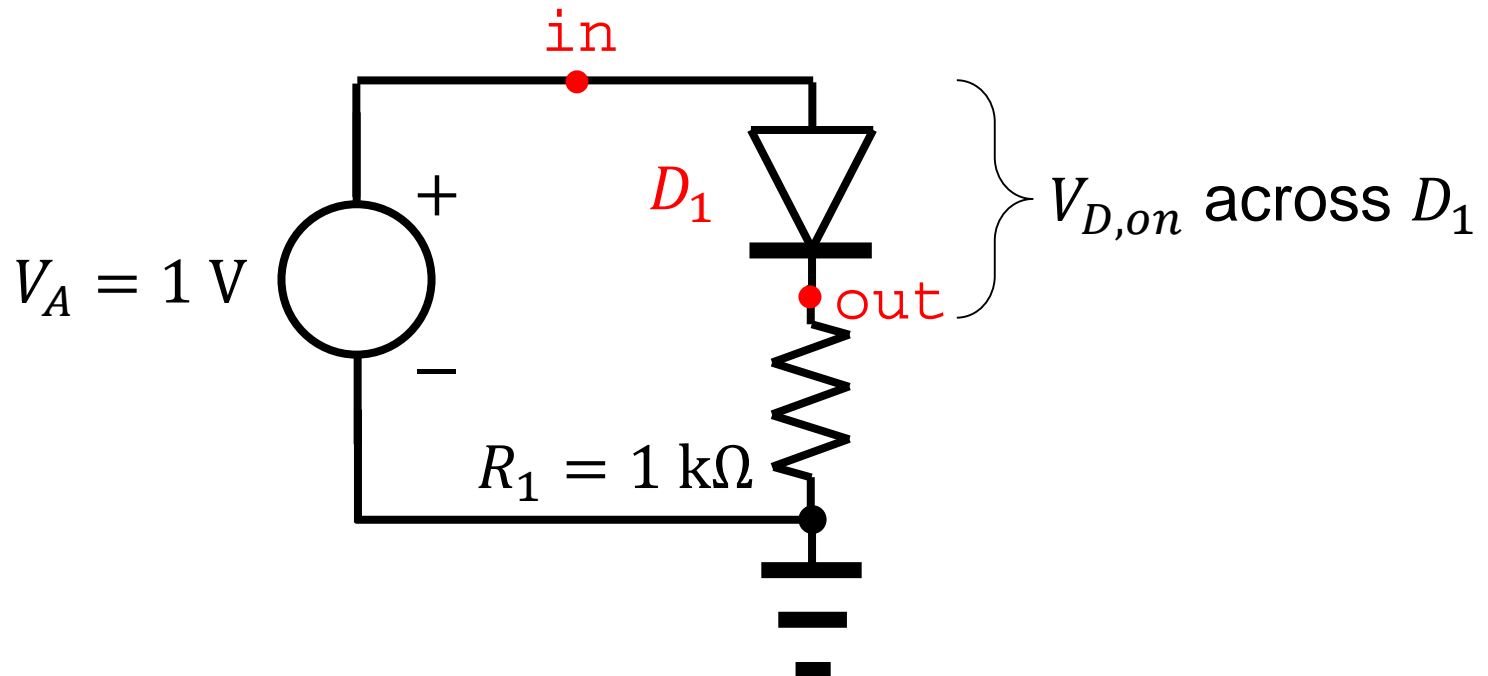- Assume that the diode is turned on.
 - Then, the diode can conduct a large current.
 - Calculate V_{out} . Obviously, it must be $1\text{ V} - V_{D,on}$.
 - Then, is it 0.3 V ? Or 0.2 V ? It depends on $V_{D,on}$.
 - The current would be around $0.2\text{ mA} \sim 0.3\text{ mA}$.



Even better job?

- We know where the solution is. (You don't start from 1 V.)

