 


Due: 23:55, June 12 (Friday night)

We have 10 problems.

In your answer file, specify both the **SOLUTION PROCEDURE** and the **FINAL SOLUTION**.

1. Calculate the small-signal voltage gain of a common-source amplifier with a correct sign. The threshold voltage of the transistor is 0.4 V.  $\mu_n C_{ox} = 400 \mu\text{A}/\text{V}^2$ . Its width is ten-times wider than its length. Neglect the channel-length modulation. Also, let  $V_{DD} = 1.8 \text{ V}$ ,  $R_D = 17.5 \text{ k}\Omega$ , and  $V_{GS} = 0.6 \text{ V}$ .
2. Calculate the dc power dissipation of the common-source amplifier in the Problem #1.
3. Consider the amplifier in the Problem #1. Estimate the maximum amplitude of a sinusoidal small-signal gate voltage to keep the MOSFET in the saturation region.
4. Calculate the (time-averaged) ac power dissipation by  $R_D$  in the Problem #1. Use the small-signal amplitude of the gate voltage, which is obtained in the Problem #3.
5. A common-gate amplifier using an NMOS transistor for which  $g_m = 4 \text{ mA/V}$  has a  $5 \text{ k}\Omega$  drain resistance and a  $5 \text{ k}\Omega$  load resistance. (Neglect the channel-length modulation.) The amplifier is driven by a voltage source having a  $500 \Omega$  resistance. What is the overall voltage gain? Note that the input signal voltage is different from the source terminal voltage in this problem.
6. Design a source follower. The output resistance of the source follower should be  $200 \Omega$ . The MOSFET has  $\mu_n C_{ox} = 400 \mu\text{A}/\text{V}^2$  and is operated at  $V_{GS} - V_{TH} = 0.25 \text{ V}$ . Find the required W/L ratio. Also specify the dc bias current.
7. In the lecture, we didn't consider a circuit topology wherein the input is applied to the drain and the output is sensed at the source. In this problem, we consider such a circuit topology.  $V_G$  is constant. Assume that the MOSFET has an output resistance of  $r_O$ . Also the transconductance is denoted as  $g_m$ . Express the voltage gain in terms of  $g_m$ ,  $r_O$ , and  $R_S$ .



8. Calculate the input and output impedances of the circuit in the Problem #7.

9. Design an NMOS inverter. The power supply  $V_{DD} = 2.5$  V. When the input voltage is  $V_{DD}$ , the output voltage is 0.1 V and the current is  $50 \mu\text{A}$ . Let the transistor be specified to have  $V_{TH} = 0.5$  V and  $\mu_n C_{ox} = 125 \mu\text{A}/\text{V}^2$ . Neglect the channel-length modulation. Specify the required values of  $W/L$  and  $R_D$ .

10. Consider the NMOS inverter in the Problem #9. A load capacitor is 45 fF. Initially, the input voltage is  $V_{DD}$ . At  $t=0$ , the input voltage suddenly becomes 0 V. Calculate the time required for the output voltage to be 1.3 V.