

---

# Lecture23:


## NMOS inverter (3)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
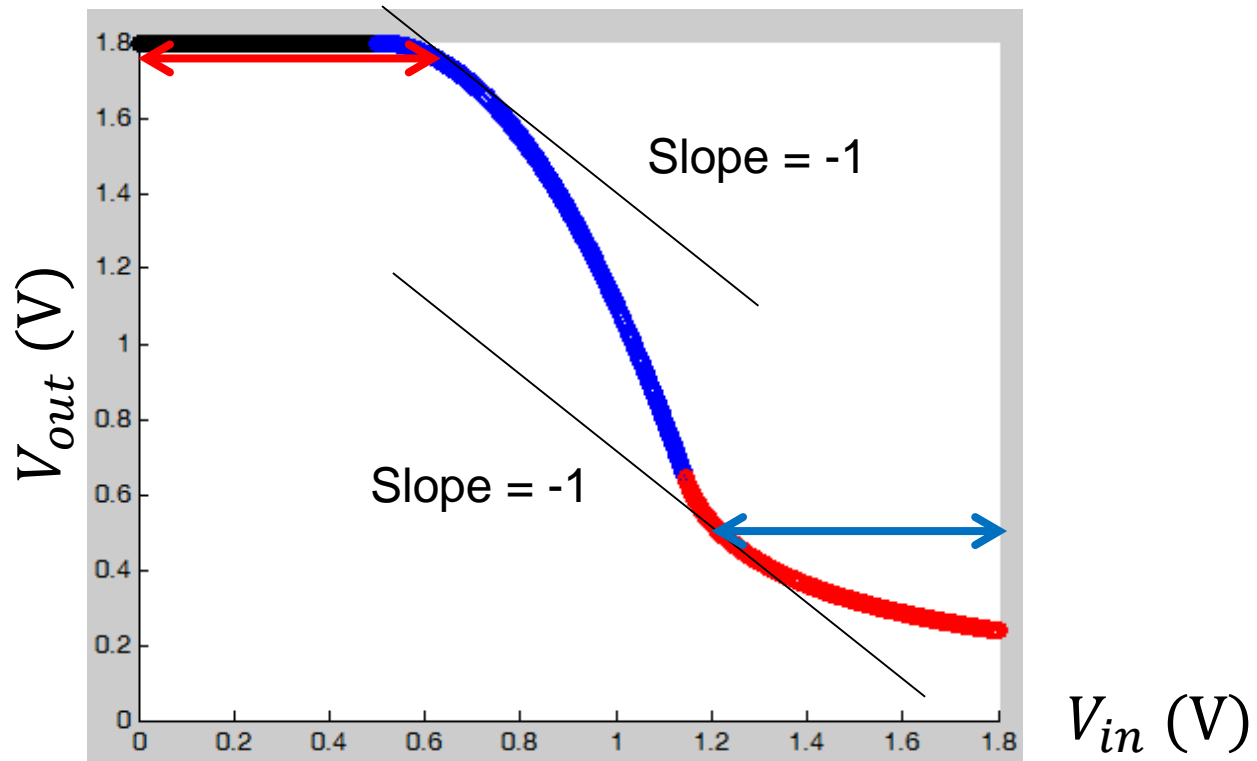
# Noise margin

- Verbatim
  - “(It) is the maximum amount of degradation (noise) at the input that can be tolerated before the output is affected significantly.”



# Noise margin of CS stage

---

- Let's calculate  $NM_L = V_{IL}$ .

- In this case, (blue curve)

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})^2$$

- Taking the differentiation w. r. t.  $V_{in}$ ,

$$\frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})$$


- At  $V_{in} = V_{IL}$ , the slope becomes -1,

$$NM_L = V_{IL} = \frac{1}{\mu_n C_{ox} \frac{W}{L} R_D} + V_{TH}$$

- (Stronger NMOS yields a reduces  $NM_L$ .)
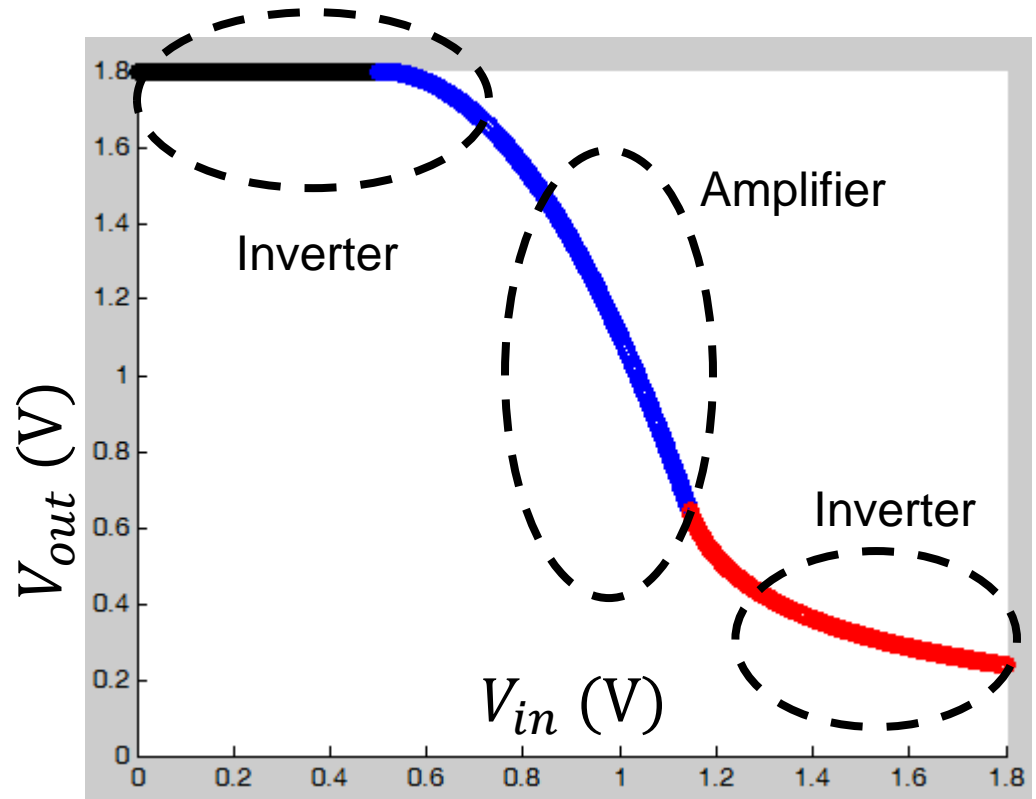
# Common-source

- Common-source configuration
  - It can be used as an inverter.
  - It can be used as an amplifier.
  - $\frac{dV_{out}}{dV_{in}}$  is the voltage gain.



# RC circuit

---


- Consider a serial RC circuit.

- The KCL states

$$\frac{V_{out} - V_{in}}{R} + C \frac{dV_{out}}{dt} = 0$$

- Assume a step-wise change of  $V_{in}$  at  $t = 0$ . It becomes  $V_{DD}$ .
- Initial output voltage is  $V_0$ .
- Its solution is given by

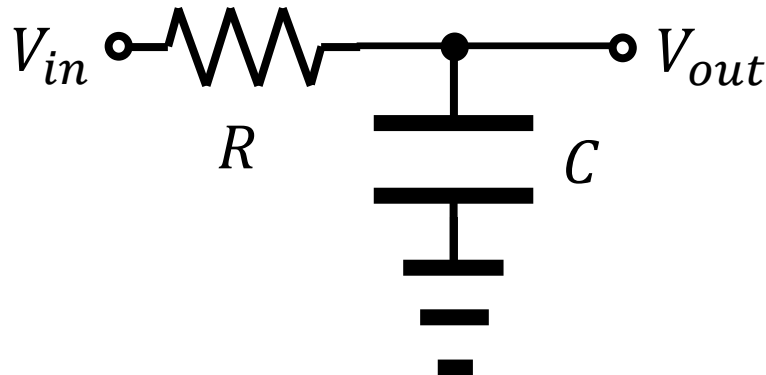
$$V_{out}(t) = V_{DD} + (V_0 - V_{DD}) \exp\left(-\frac{t}{RC}\right)$$


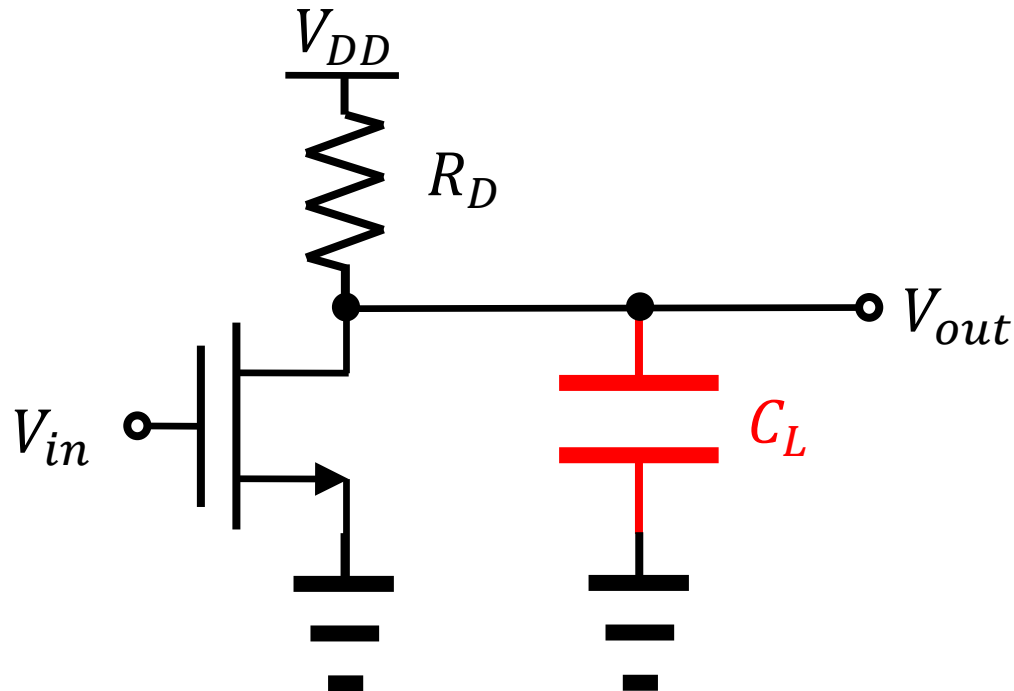
# Speed of inverter (1/4)

---


- VTC merely describes the DC behavior.
  - Input voltages with different frequencies (1 kHz, 1 MHz, 1 GHz, ...)
  - Time-dependent behavior


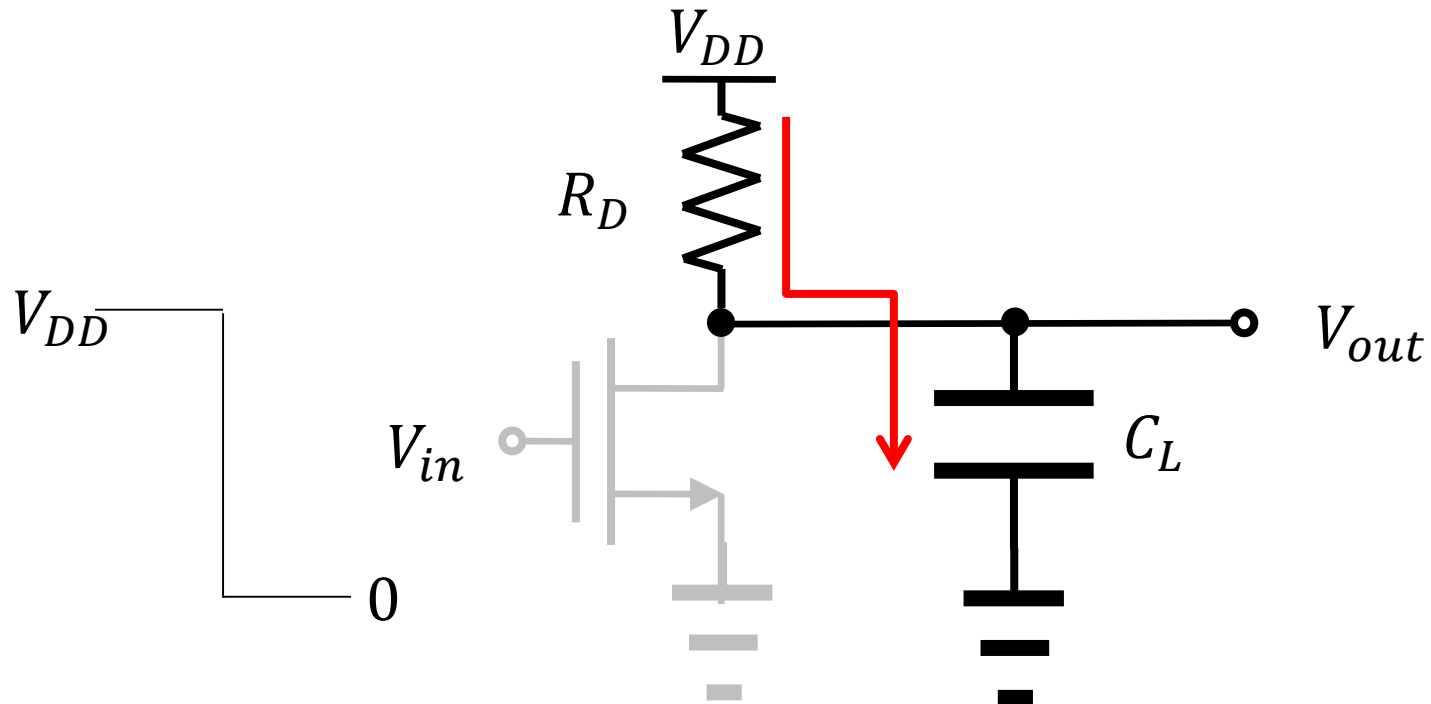
# Speed of inverter (2/4)

---

- A rapid transition of  $V_{in}$  from  $V_{DD}$  to 0
  - The capacitor should be charged.



# Speed of inverter (3/4)

---

- Simply, it is a RC circuit.

- Then, the solution is simply

$$V_{out}(t) = V_{out}(0^-) + [V_{DD} - V_{out}(0^-)] \left( 1 - \exp \frac{-t}{R_D C_L} \right)$$

- Since  $\exp(-3) \approx 0.05$ , after  $3R_D C_L$ ,  $V_{out}$  reaches  $0.95 V_{DD}$ .
    - Yes, it takes time to get the stable output voltage...
    - The delay restricts the maximum signal frequency.




# Speed of inverter (4/4)

---

- A rapid transition of  $V_{in}$  from 0 to  $V_{DD}$  to 0
  - At the initial phase, the resistor does not conduct.
  - Also the MOSFET is operated in its saturation mode. Then,

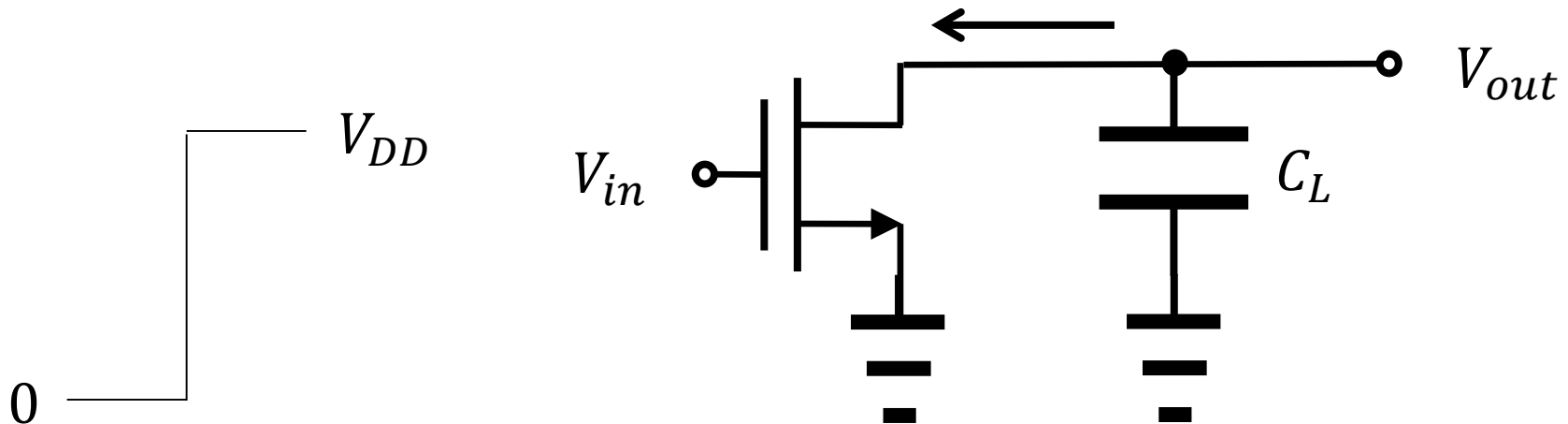
$$I_{D,sat} + C_L \frac{dV_{out}}{dt} = 0$$


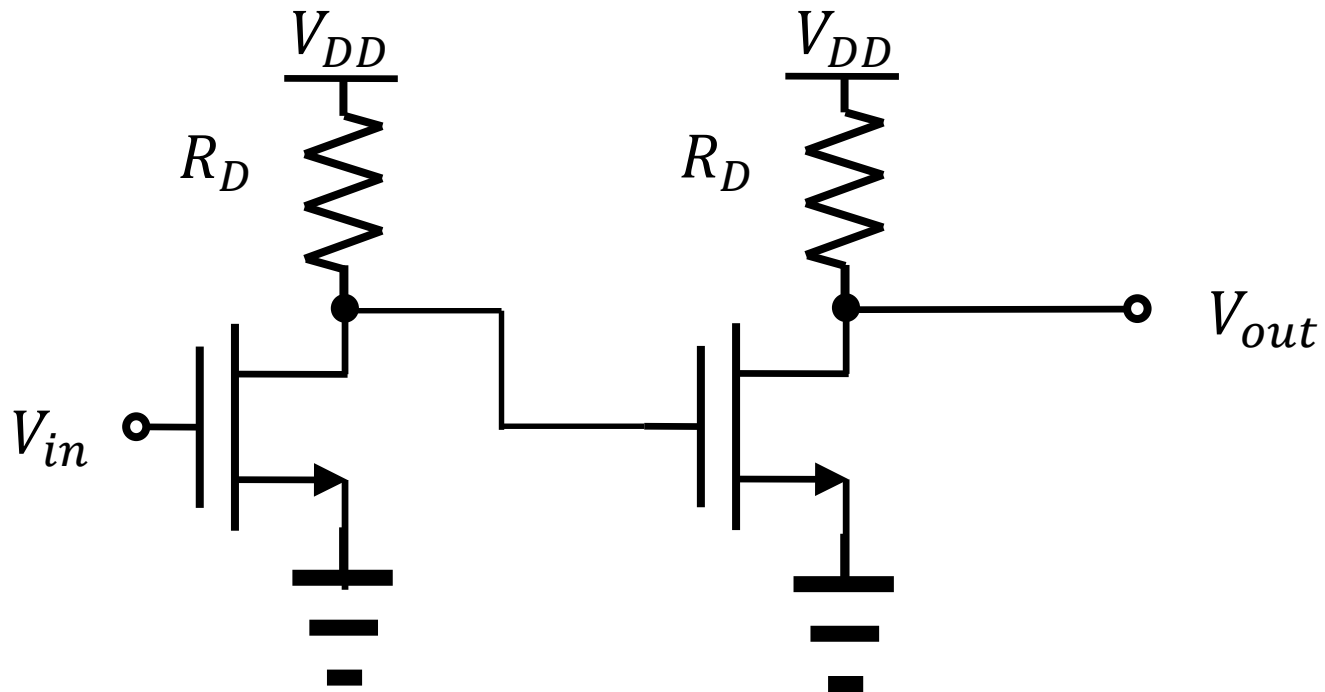
# Origin of $C_L$ ?

---

- Consider an inverter chain.
  - Then, what is the load capacitance for the first stage?




- Interconnect

# Standby(!) power

---

- The biggest problem in the NMOS inverter
  - When  $V_{in} = 0$ , no standby power
  - When  $V_{in} = V_{DD}$ ?
  - The power consumption is (approximately)  $\frac{V_{DD}^2}{R_D}$ .
  - If  $V_{DD} = 1.8\text{ V}$  and  $R_D = 10\text{ k}\Omega$ ,  
324  $\mu\text{W}$ !
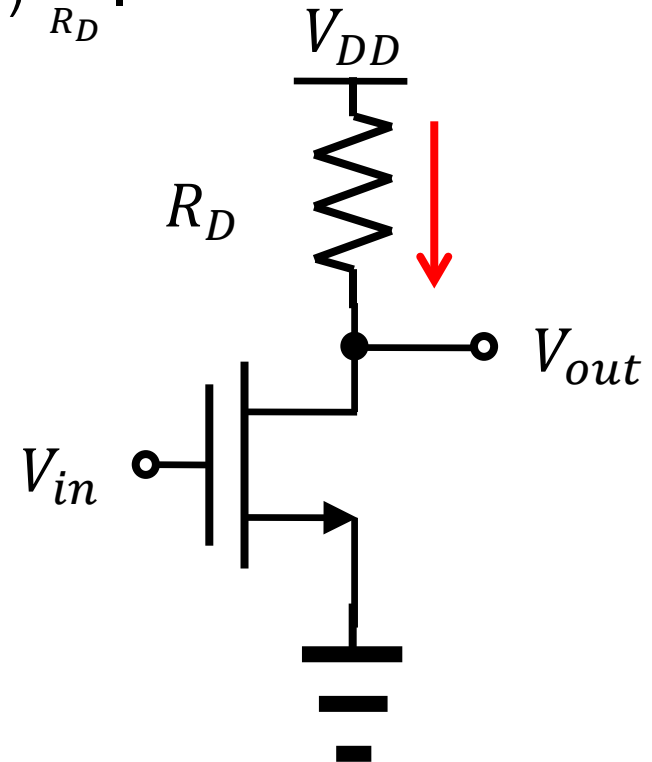
$$I_D = \frac{V_{DD} - V_{out}}{R_D} \approx \frac{V_{DD}}{R_D}$$



# NMOS inverter

- Passive “pull-up” device

- (a) Degradation of output level

Too small  $R_D$ , when  $V_{in} = V_{DD}$ .

In this case, large  $R_D$  is desirable.

- (b) Risetime limitation

Too small current for  $1 \rightarrow 0$  transition. ( $V_{in} = 0$ )


In this case, a better capability to charge the  $C_L$  is desirable.

- (c) Static power consumption

No ability to block the current, when  $V_{in} = V_{DD}$ .

In this case, no current conduction is desirable.


- (a) & (c)  $\leftrightarrow$  (b)

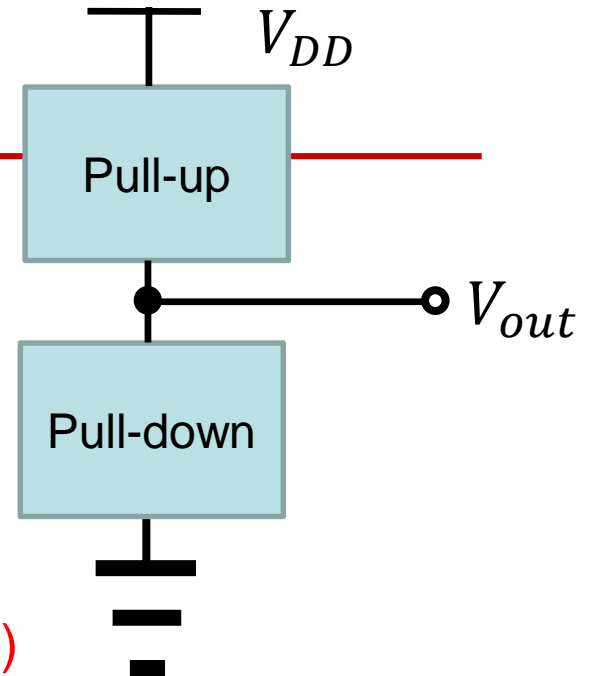
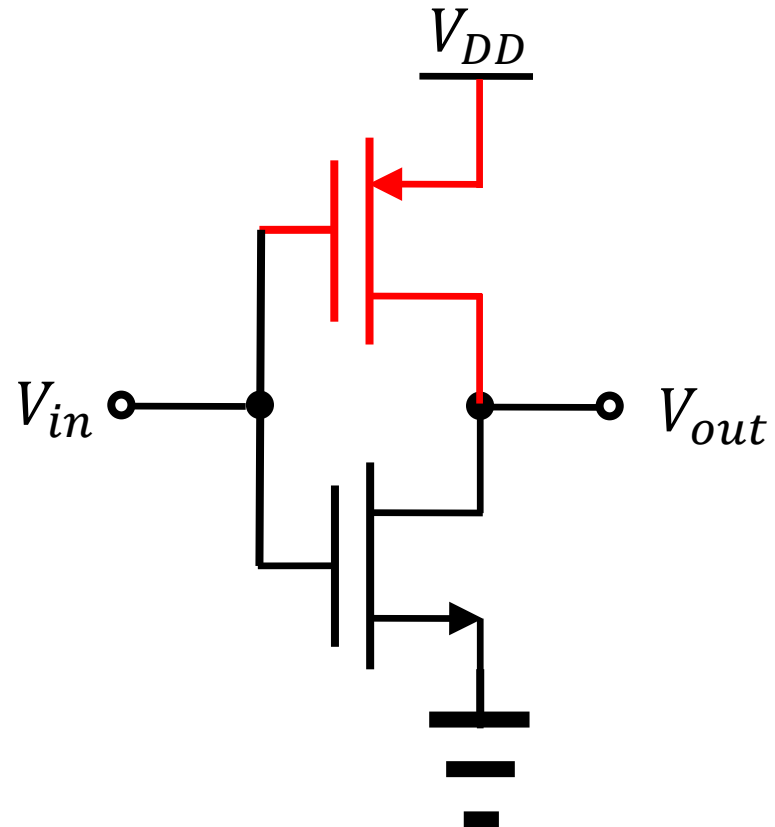
# CMOS inverter


---

- Ideal “pull-up” should have the following properties.
  - When  $V_{in} = V_{DD}$ , no current conduction.
  - When  $V_{in} = 0$ , improved current conduction.
- PMOS can do those jobs!




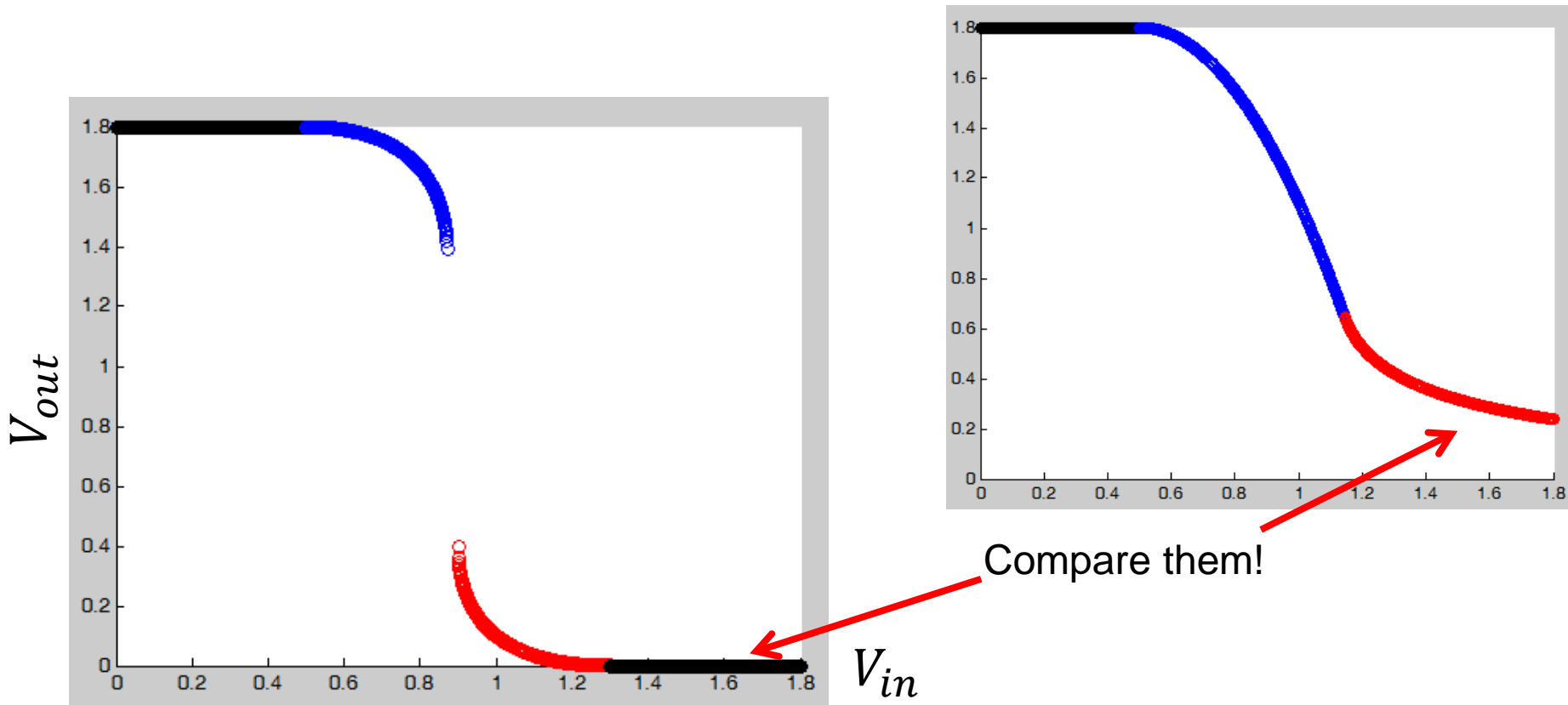
# CMOS inverter

- Voltage transfer curve of a CMOS inverter



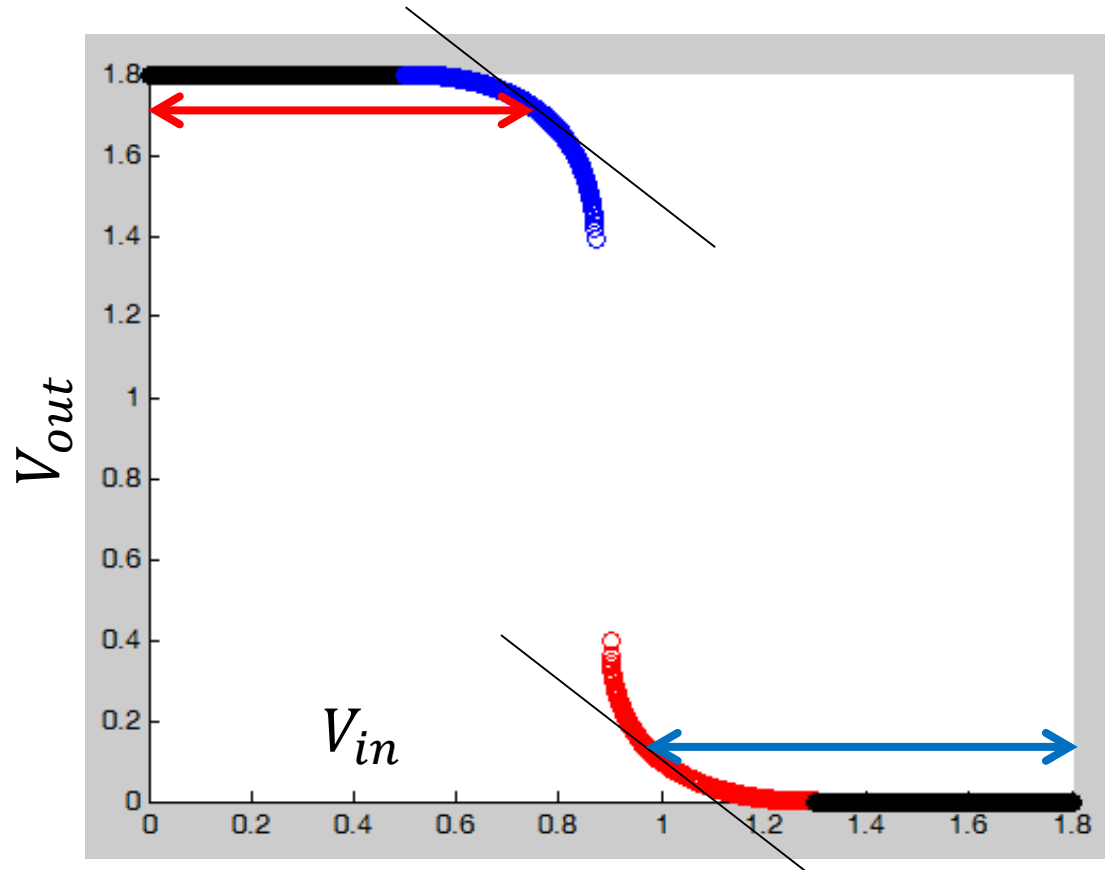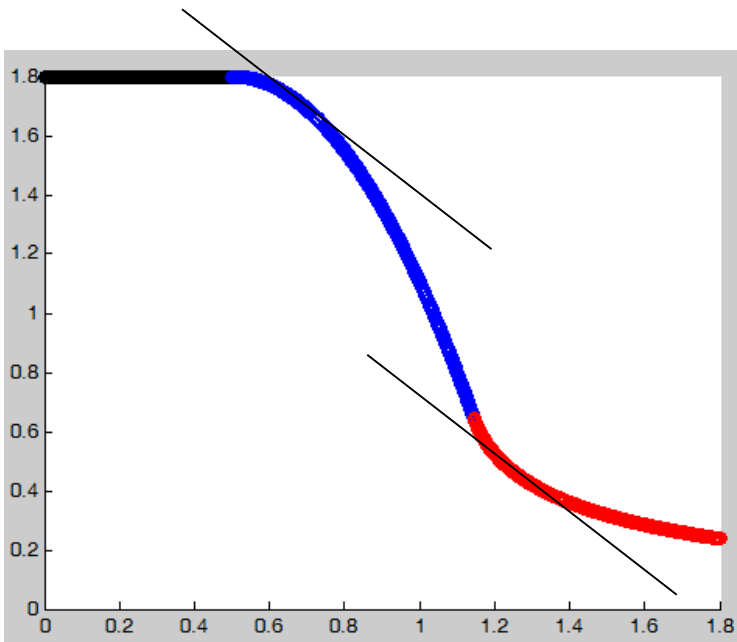
# Noise margin?

- Greatly improved!
  - Steeper transition


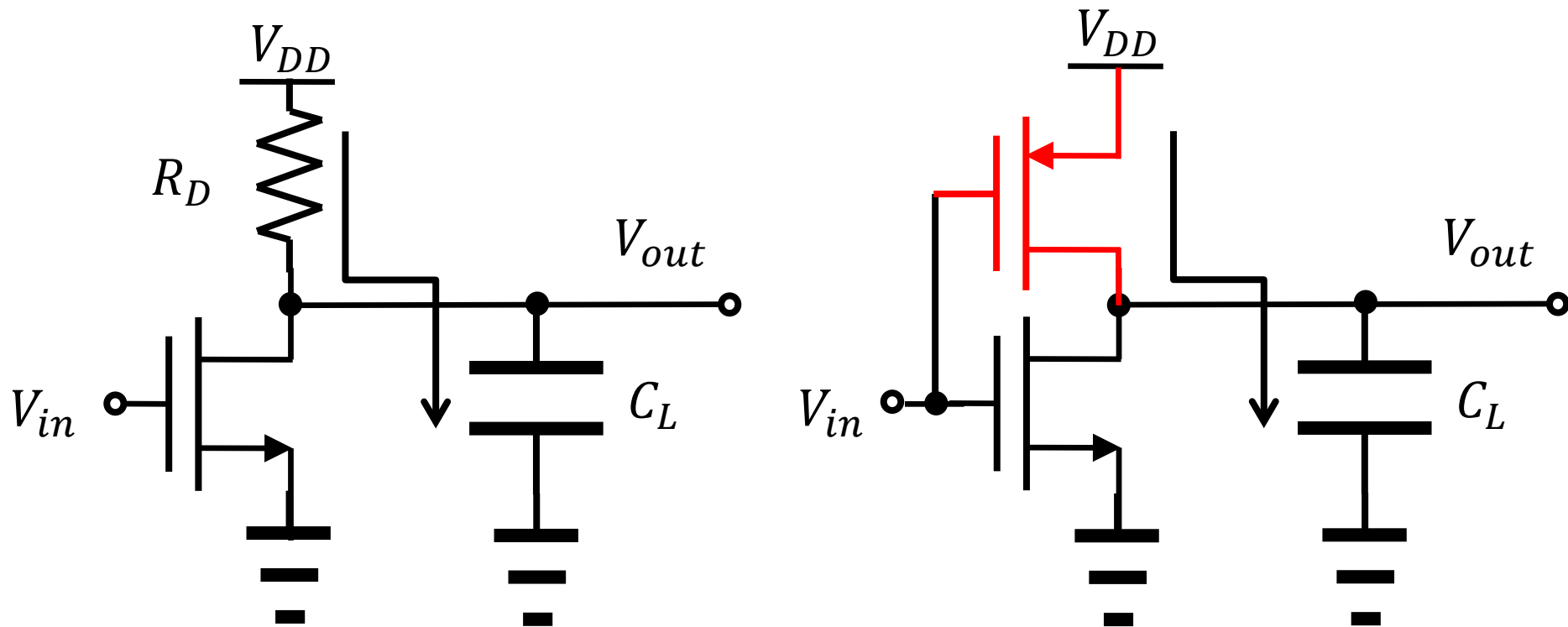
# Speed of CMOS inverter (1/4)


- Consider the input transition from HIGH to LOW.
  - Instead of the resistor ( $R_D$ ), now the PMOS pulls up the  $V_{out}$ .




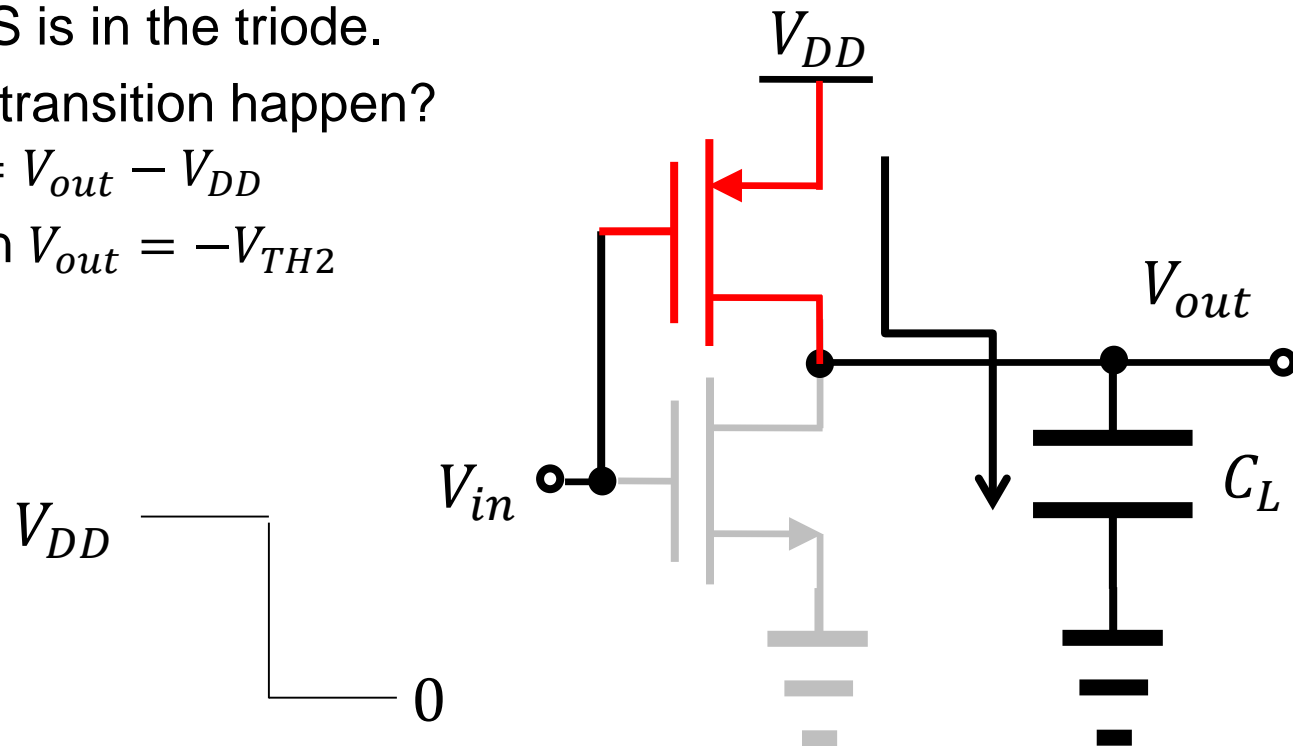
# Speed of CMOS inverter (2/4)

- Guess the charging speed.
  - The PMOS current matters. ( $I_{PMOS} = C_L \frac{dV_{out}}{dt}$ )
  - Initially, the PMOS is in the saturation.
  - Later, the PMOS is in the triode.
  - When does the transition happen?  
 $V_{in} - V_{DD} - V_{TH2} = V_{out} - V_{DD}$
  - Therefore, when  $V_{out} = -V_{TH2}$




# Speed of CMOS inverter (3/4)

---

- The first case (charge up to  $-V_{TH2}$ )
  - PMOS saturation current (constant)

$$T_{PLH1} = \frac{C_L |V_{TH2}|}{\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{DD} - |V_{TH2}|)^2}$$

$$T_{PLH1} = R_{on2} C_L \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|}$$

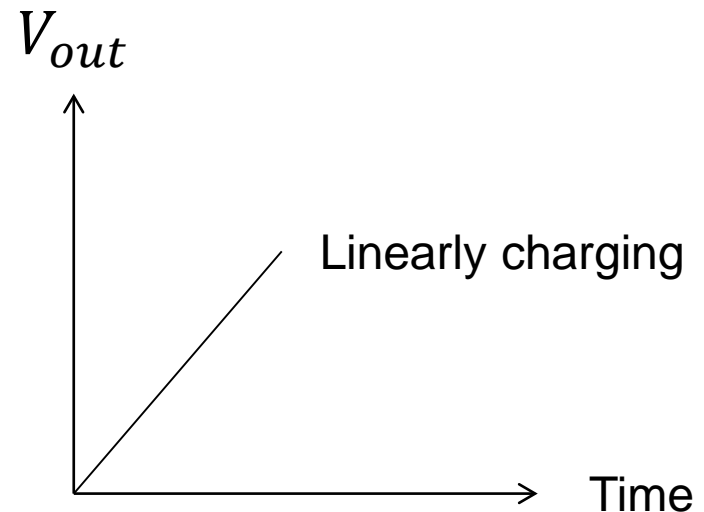

# Speed of CMOS inverter (4/4)

---

- The second case (charge up to  $\frac{V_{DD}}{2}$ )
  - PMOS triode current
$$\frac{1}{2} \mu_p C_{ox} \frac{W}{L} [2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2] = C_L \frac{dV_{out}}{dt}$$
  - Time to reach  $\frac{V_{DD}}{2}$ 
$$T_{PLH2} = R_{on2} C_L \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right)$$
- The overall propagation delay is
  - $T_{PLH} = R_{on2} C_L \left[ \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$

# Power consumption

---

- No static power dissipated!
  - Only the “dynamic” power dissipation is determined.
  - High → Low → High → ...
  - It involves charging and discharging the load capacitance.
  - The energy stored in the load capacitance

$$\frac{1}{2} C_L V_{DD}^2$$

- The energy dissipated by the PMOS is also  $\frac{1}{2} C_L V_{DD}^2$ .
- Therefore,  $C_L V_{DD}^2$  is dissipated during  $T_{in}$ .

$$P_{av} = f_{in} C_L V_{DD}^2$$