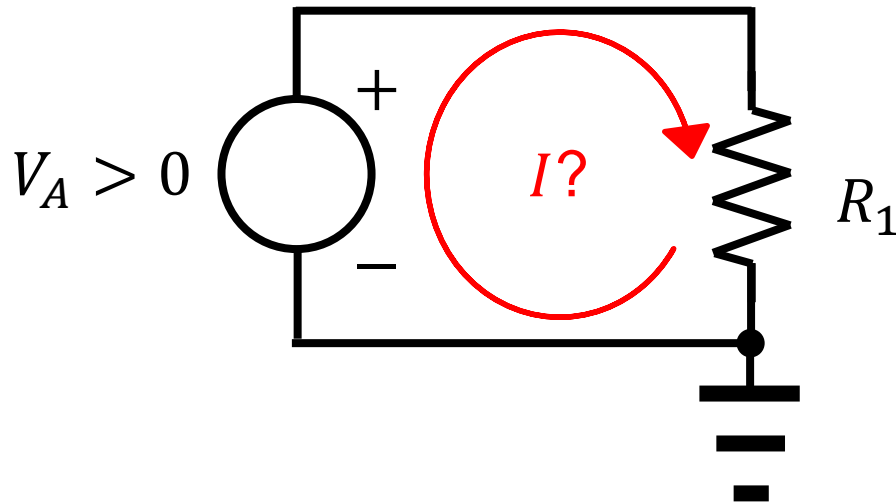

Lecture2: Circuit theory

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

A simple problem


- Solve the problem.
 - What is the loop current?



- It is an easy problem.


Elements

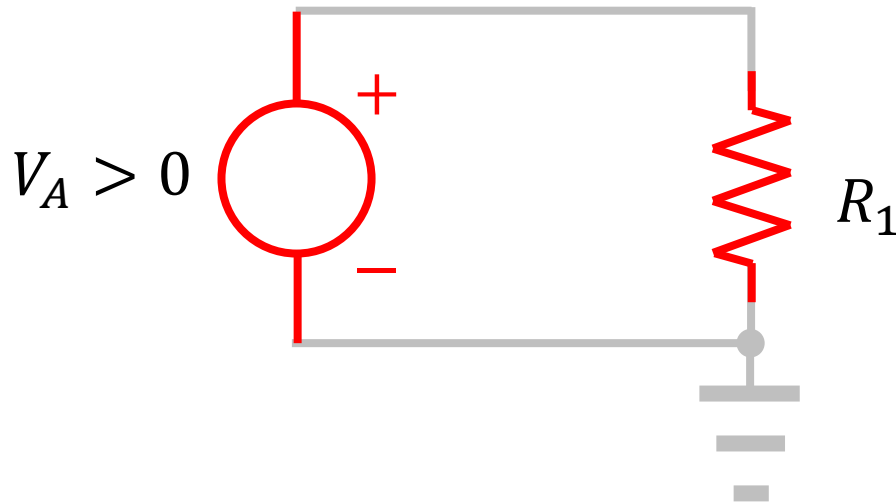- Resistors, capacitors, etc
 - They can have multiple terminals.
 - A resistor has two terminals.
 - A diode has two terminals.
 - A MOSFET has three (or four) terminals.




Convention for current

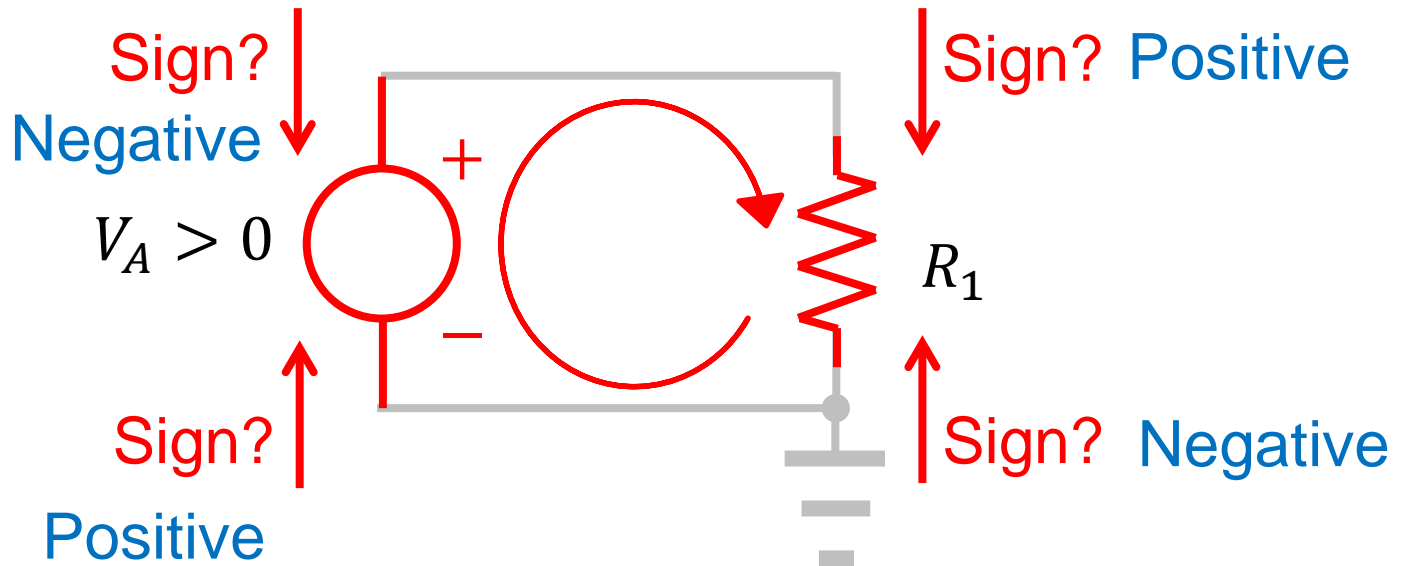- Terminal current
 - When the current flows into the element, the terminal current is positive.



Nodes

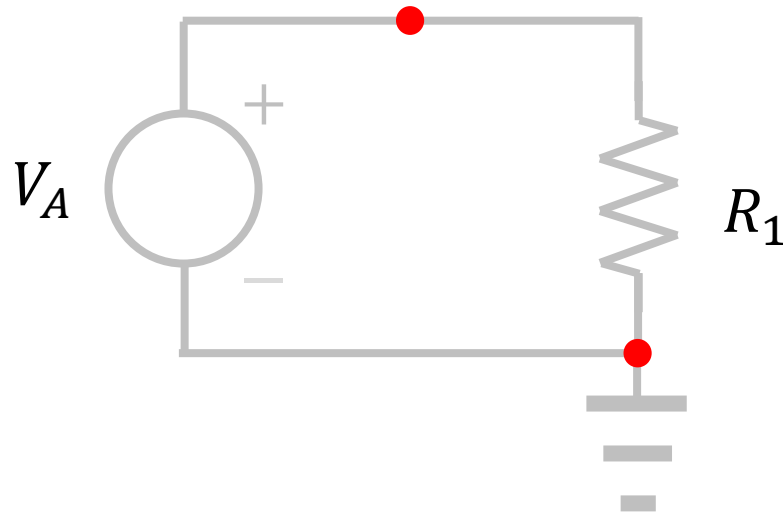
- A point to which multiple terminals are tied.
 - Usually, a dot is used to represent a node.
 - There is a special node, GND.



How to describe a circuit

- Of course, we can draw a circuit schematic. What else?
- A netlist for this circuit looks like:

```
va out 0 1.0  
r1 out 0 1000
```

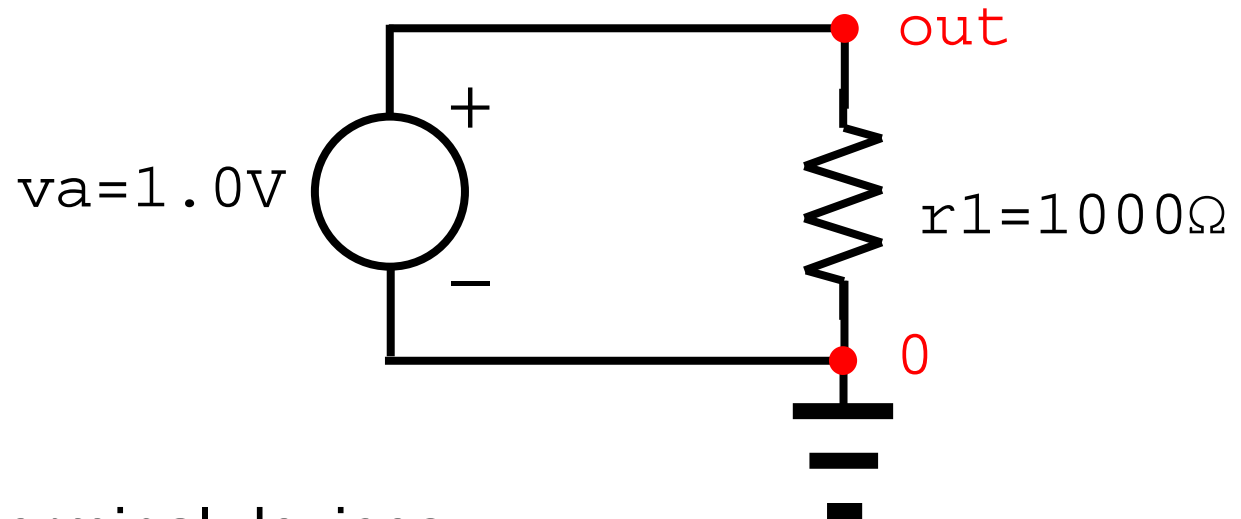

- Format for two-terminal devices
elementlabel node1 node2 value


From netlist to schematic

- Assume that we have only a netlist.

```
va out 0 1.0
```

```
r1 out 0 1000
```

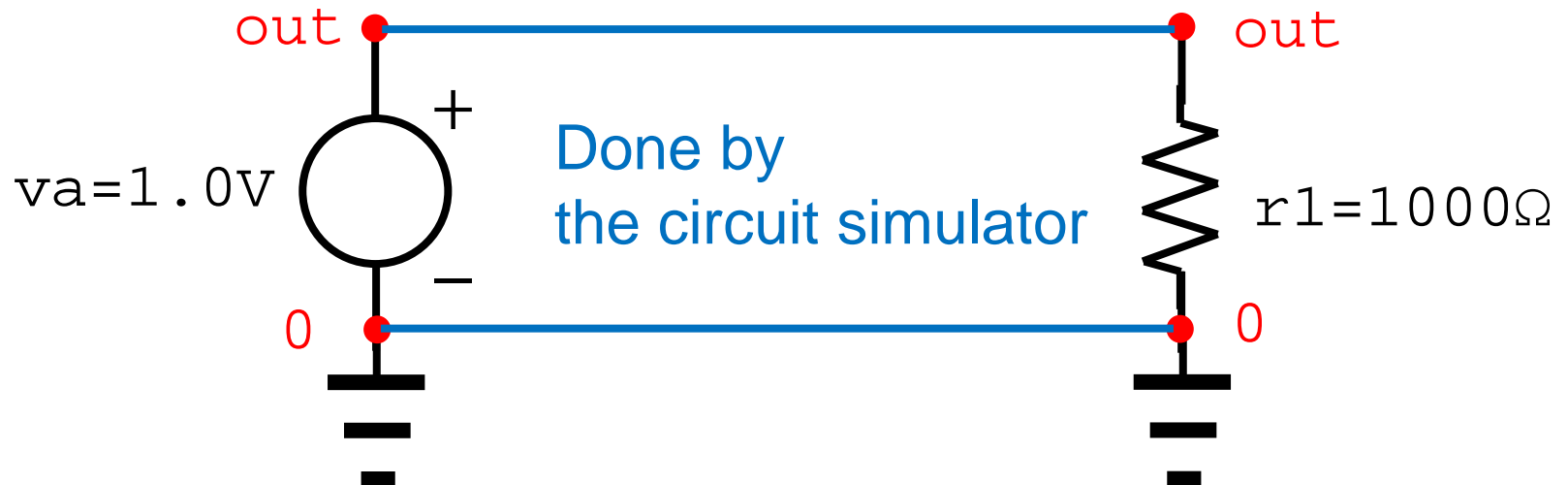- Let's draw the schematic.
 - The first line gives us a voltage source.
 - The second a resistor.




RC filter

- A netlist for this circuit looks like:

```
c1 in out 5e-12
```

```
r1 out 0 2e6
```

```
vin in 0 1.5
```

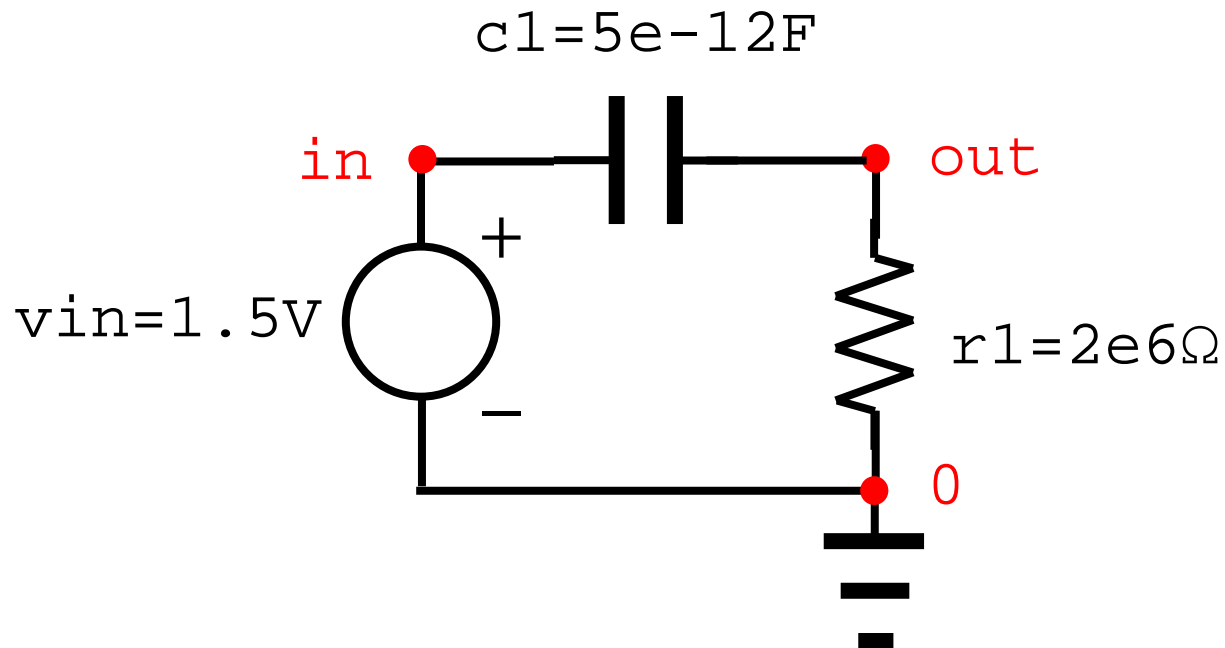

Two-terminal elements

- Consider a two-terminal element.
 - Then, we want to know I_1 , I_2 , V_1 , and V_2 .
 - We have four unknowns, therefore, we need four equations.
 - Three equations are obvious:
 - (Current for the terminal 1) + (Current for the terminal 2) = 0
$$I_1 + I_2 = 0$$
 - (Voltage for the terminal 1) – (Connected node voltage) = 0
 - (Voltage for the terminal 2) – (Connected node voltage) = 0
- One remaining equation is element-specific.

V, I, R, C, and L

- Voltage source

$$V_1 - V_2 = V_{source}$$

- Current source

$$I_1 = I_{source}$$

- Resistor

$$I_1 = \frac{V_1 - V_2}{R}$$

- Capacitor

$$I_1 = C \frac{d(V_1 - V_2)}{dt}$$

- Inductor


$$V_1 - V_2 = L \frac{dI_1}{dt}$$

Remaining task

- Four unknowns, four equations
 - The numbers are matched.
 - However, we must know the node voltages.
$$V_1 - (\text{Connected node voltage}) = 0$$
$$V_2 - (\text{Connected node voltage}) = 0$$
 - Therefore, we need more equations, whose number is the number of nodes.

KCL

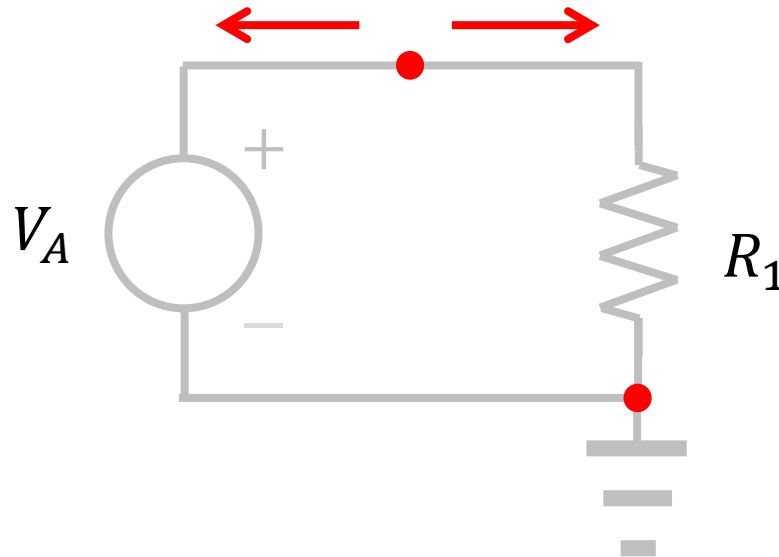
- The basic principle of circuit analysis is...
 - Kirchhoff's current law (KCL)!
 - At any node in an electrical circuit, the sum of currents flowing into that node is equal to the sum of currents flowing out of that node.



Total current density

- Why do we have the KCL?
 - The total current density is a sum of the particle current density and the displacement current density:
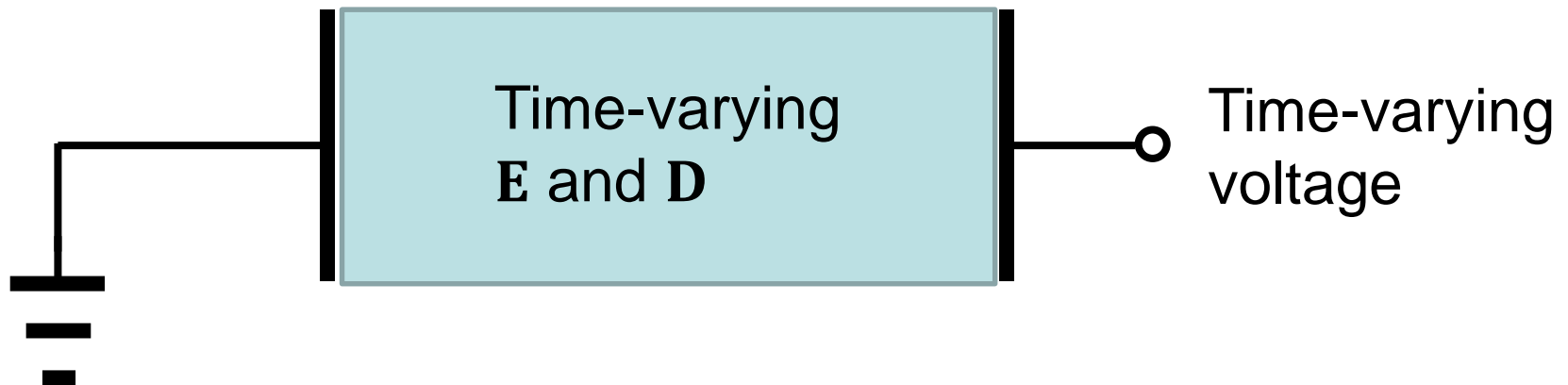
$$\mathbf{J}_{tot} = \mathbf{J}_{particle} + \frac{\partial}{\partial t} \mathbf{D}$$



- According to the Maxwell equations,

$$\nabla \cdot \mathbf{J}_{tot} = 0$$

Integration of $\nabla \cdot \mathbf{J}_{tot} = 0$

- Volume integral

- Integration over a certain volume, Ω , yields

$$\int_{\Omega} (\nabla \cdot \mathbf{J}_{tot}) d\mathbf{r} = \oint_S \mathbf{J}_{tot} \cdot d\mathbf{a} = 0$$

- Here, S is the surface of Ω .

- Branch current

- By integrating \mathbf{J}_{tot} over a certain surface, we can calculate the current through that surface.

$$\int_{A_i} \mathbf{J}_{tot} \cdot d\mathbf{a} = I_i$$


- Here, A_i is the surface of a certain branch and I_i is a branch current.

Finally,

- By combining the previous relations,
 - We have the KCL.

$$\sum_i I_i = 0$$

- Its derivation is quite general.

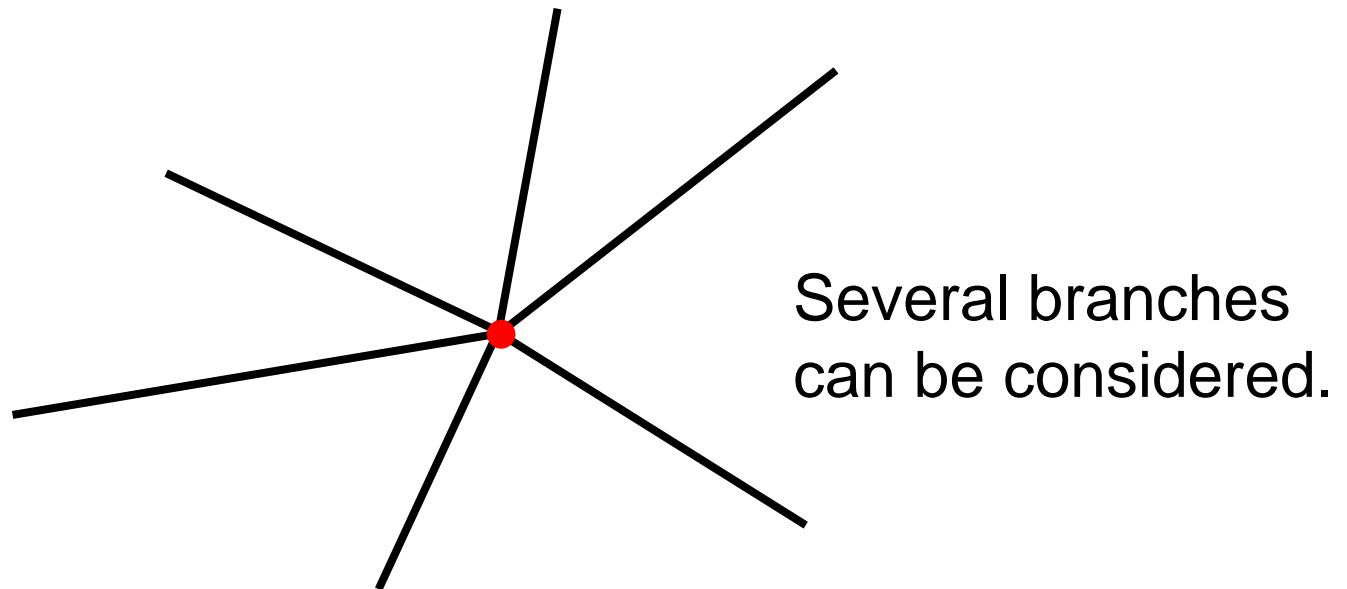


Voltage source + resistor

- Our simple problem
 - Following equations are identified.

$$I_{va} + I_{r1} = 0 \quad \text{KCL}$$

$$V(out) - 0.0 = 1.0 \quad \text{Voltage source}$$
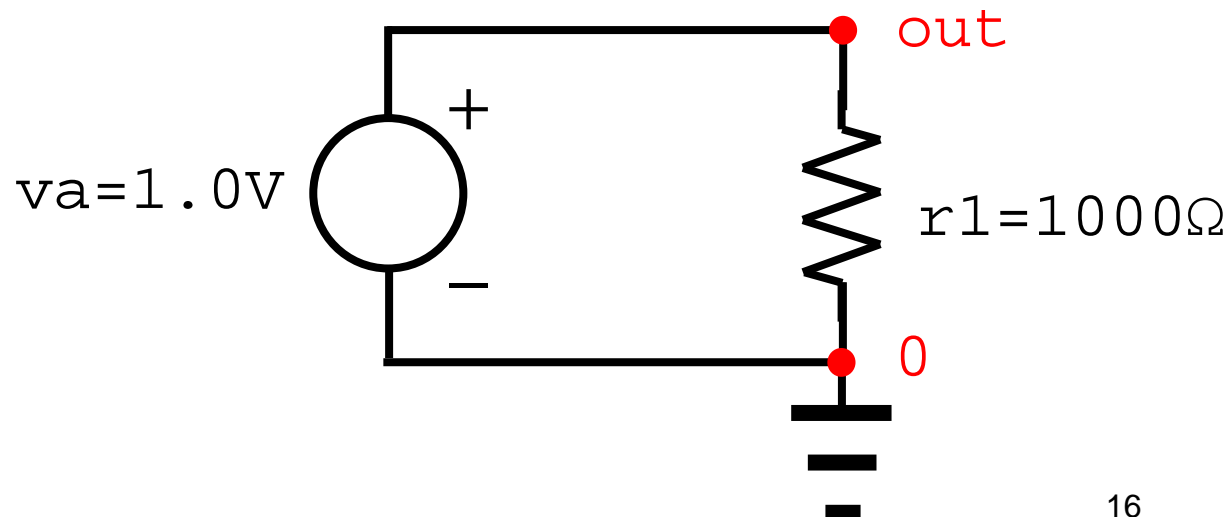
$$I_{r1} = \frac{V(out)}{1000} \quad \text{Resistor}$$



Current source + resistors

- A typical example in this course


$$I_{iin} + I_{r0} + I_{rd} = 0 \quad \text{KCL}$$

$$I_{iin} = 10^{-3} \quad \text{Current source}$$

$$I_{r0} = \frac{V(out)}{2000}$$

Resistors

$$I_{rd} = \frac{V(out)}{2000}$$

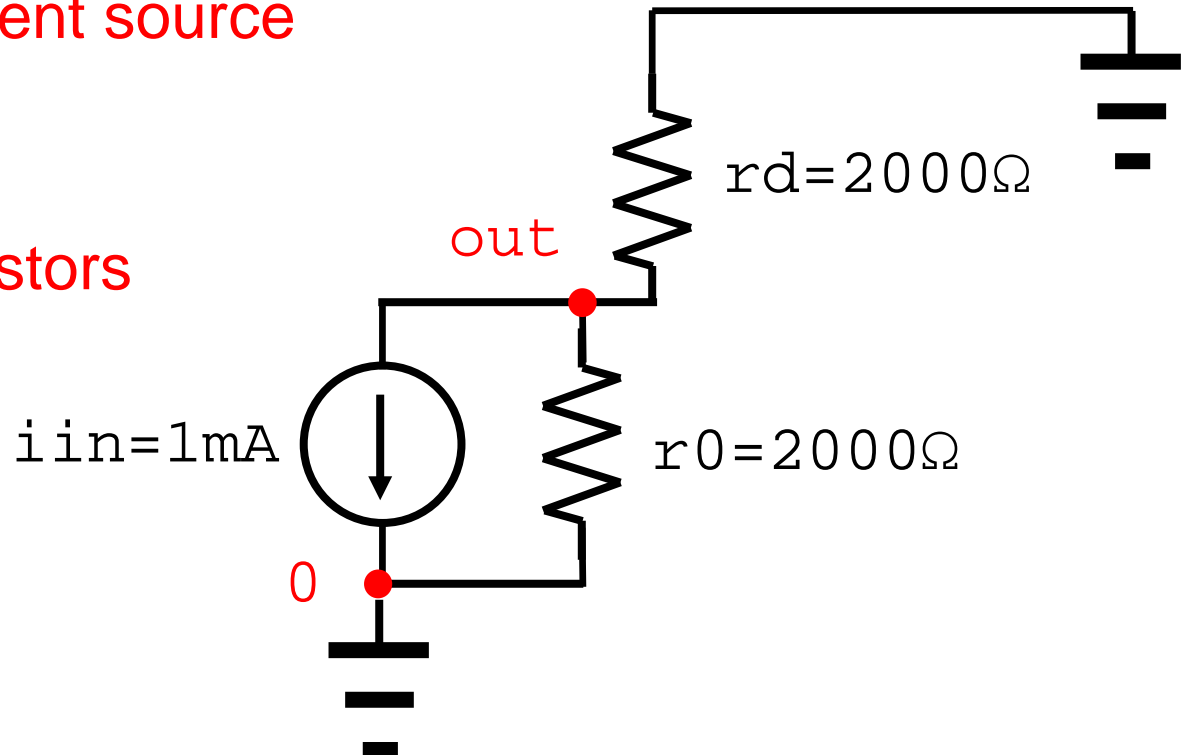

Source degeneration

- An additional resistor

