

---



# Lecture7: Diode

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

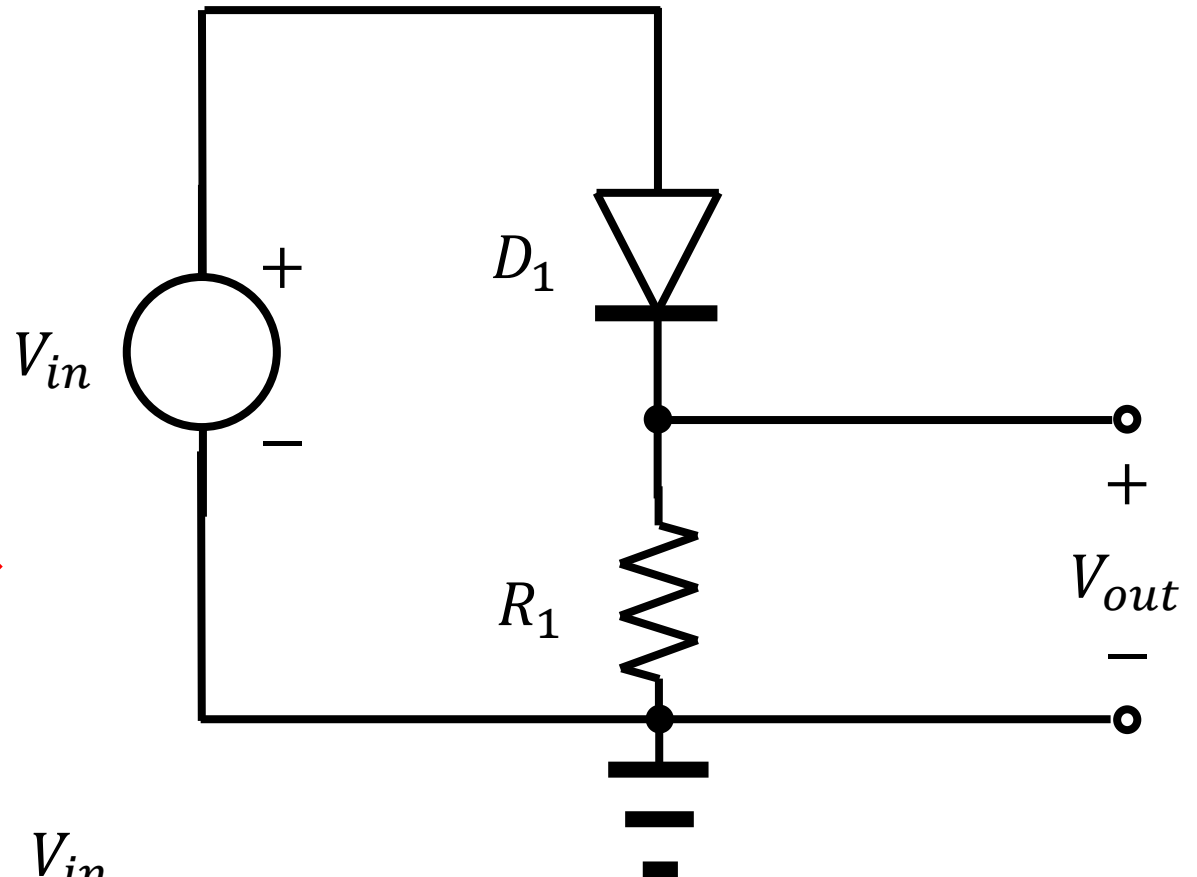
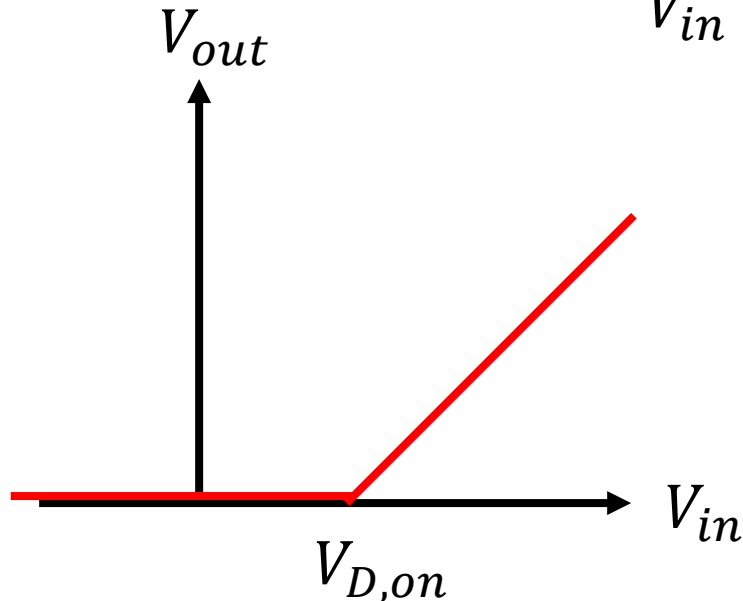
# Rectifier

- Analyze it!
  - When  $V_{in} < V_{D,on}$ ?
  - When  $V_{in} > V_{D,on}$ ?


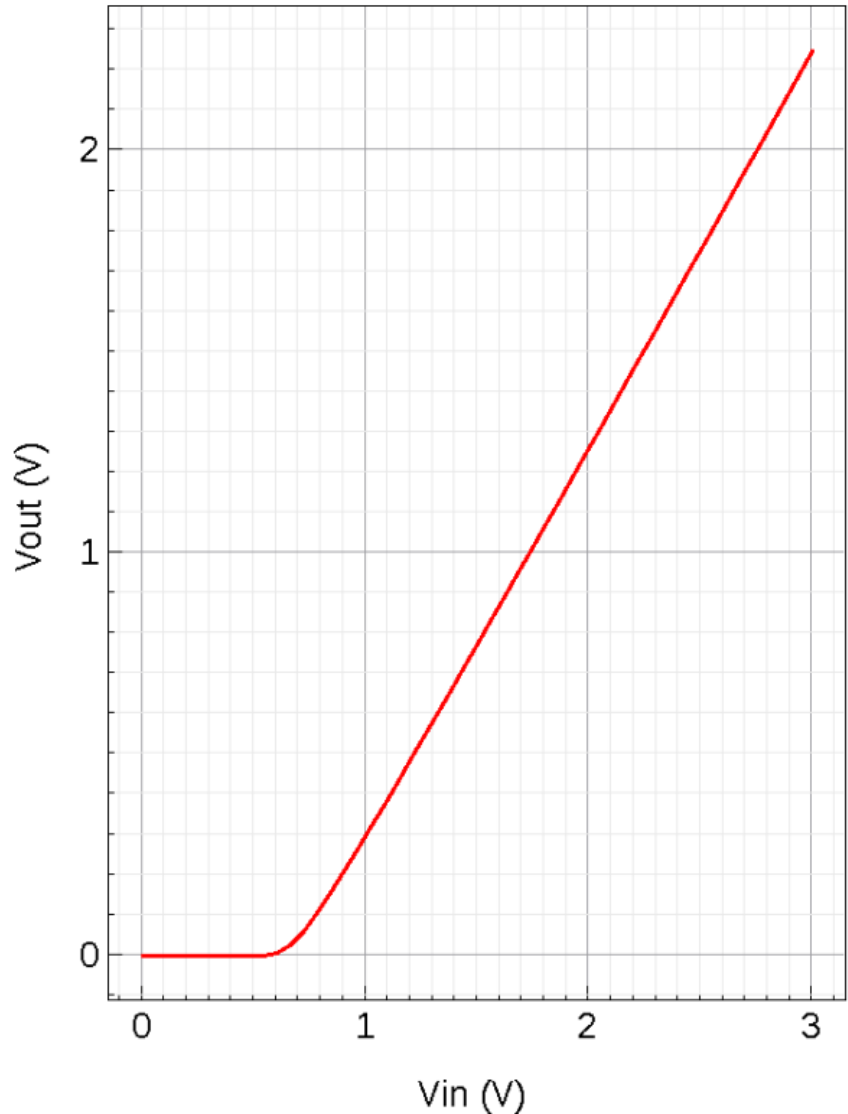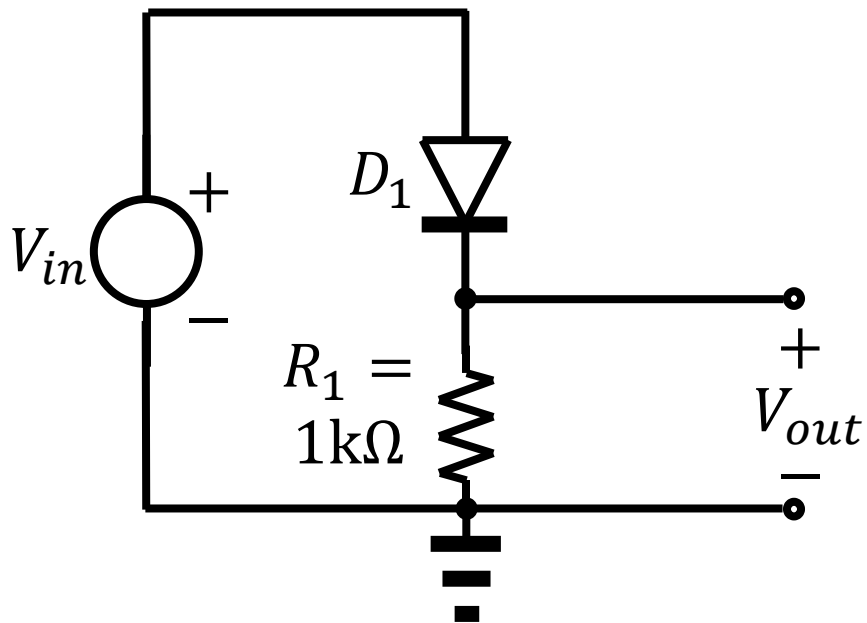
# Simulation result


- $I_S = 0.5 \text{ fA}$  and  $R_1 = 1 \text{ k}\Omega$


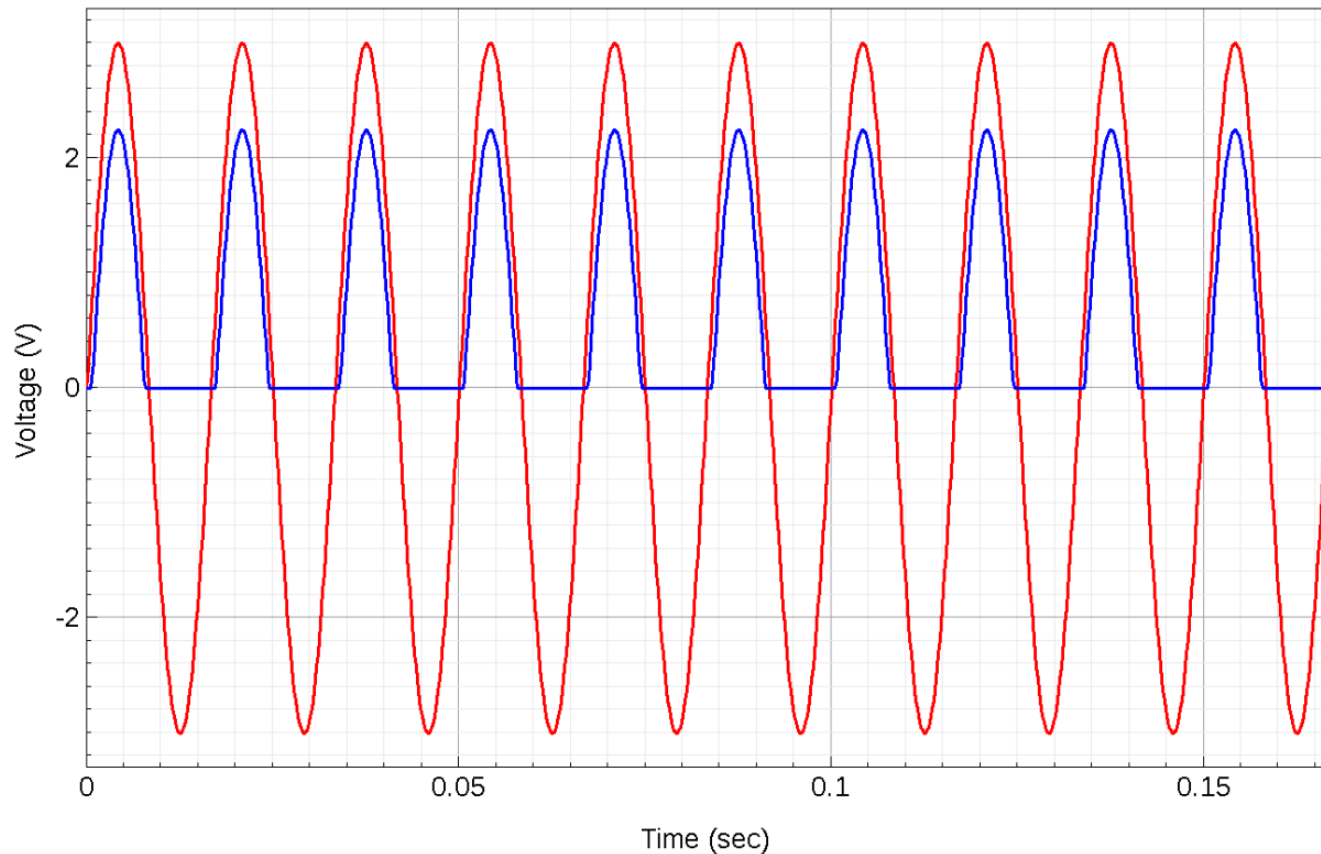
# Time-varying input voltage

---

- For example,  $V_{in}(t) = 3 \sin(2\pi ft)$  V. 60 Hz. 10 periods



# Frequency domain

---

- $V_{in}(t) = A \sin(2\pi ft)$  V and  $V_{out}(t) = A \sin(2\pi ft) u(\sin(2\pi ft))$  V

<<Frequency analysis of  $V_{in}$ >>

- Component at  $f$ :  $A$  V

<<Frequency analysis of  $V_{out}$ >>


- DC component:  $\frac{A}{\pi}$  V
- Component at  $f$ :  $\frac{A}{2}$  V
- Component at  $2f$ :  $-\frac{2A}{3\pi}$  V (For a cosine function)


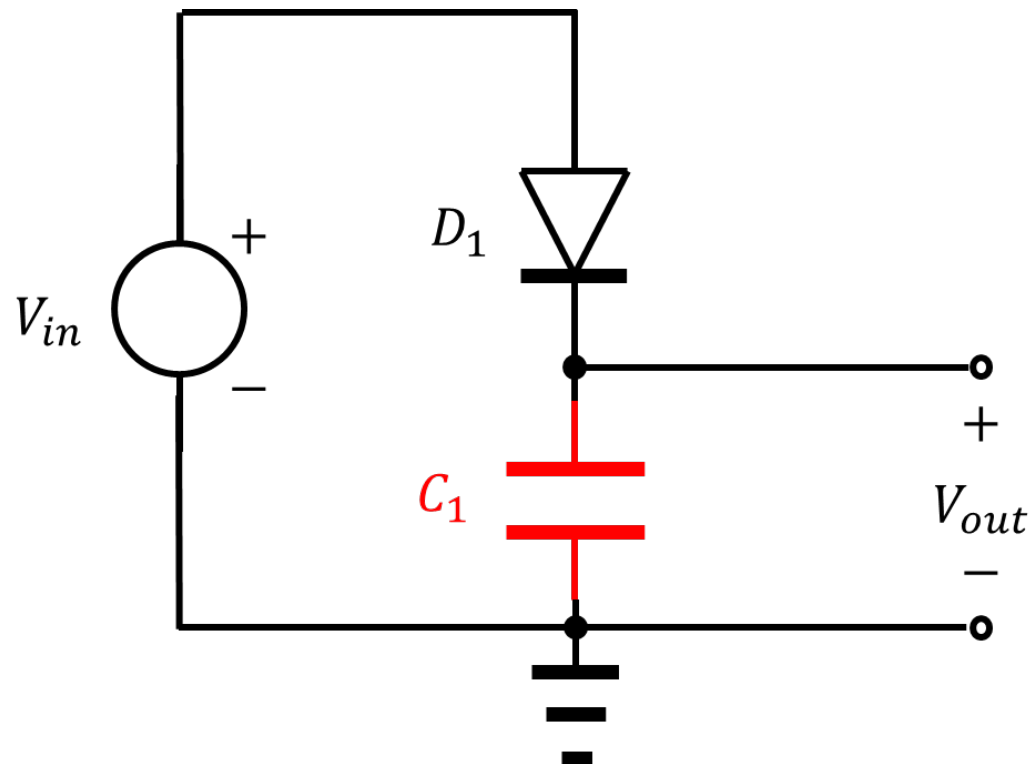
# Introducing a capacitor

---

- Difference from the previous one?
  - Assume a sinusoidal input voltage. (AC input)
  - Guess the output waveform.



# Qualitative understanding


---

- Consider the first period.
  - When the input voltage exceeds  $V_{D,on}$ , the diode is turned on.
  - The diode conducts a current.
  - The charge is stored in the capacitor. Hence, the output voltage increases.
  - When the input voltage is lower than  $V_{D,on}$ , the output voltage does not change. (*Why?*)
- After the first period...
  - In the second period, the diode current is smaller than the one in the first period. (*Why?*)
  - After some periods, the diode current vanishes.
  - A DC output voltage is established.
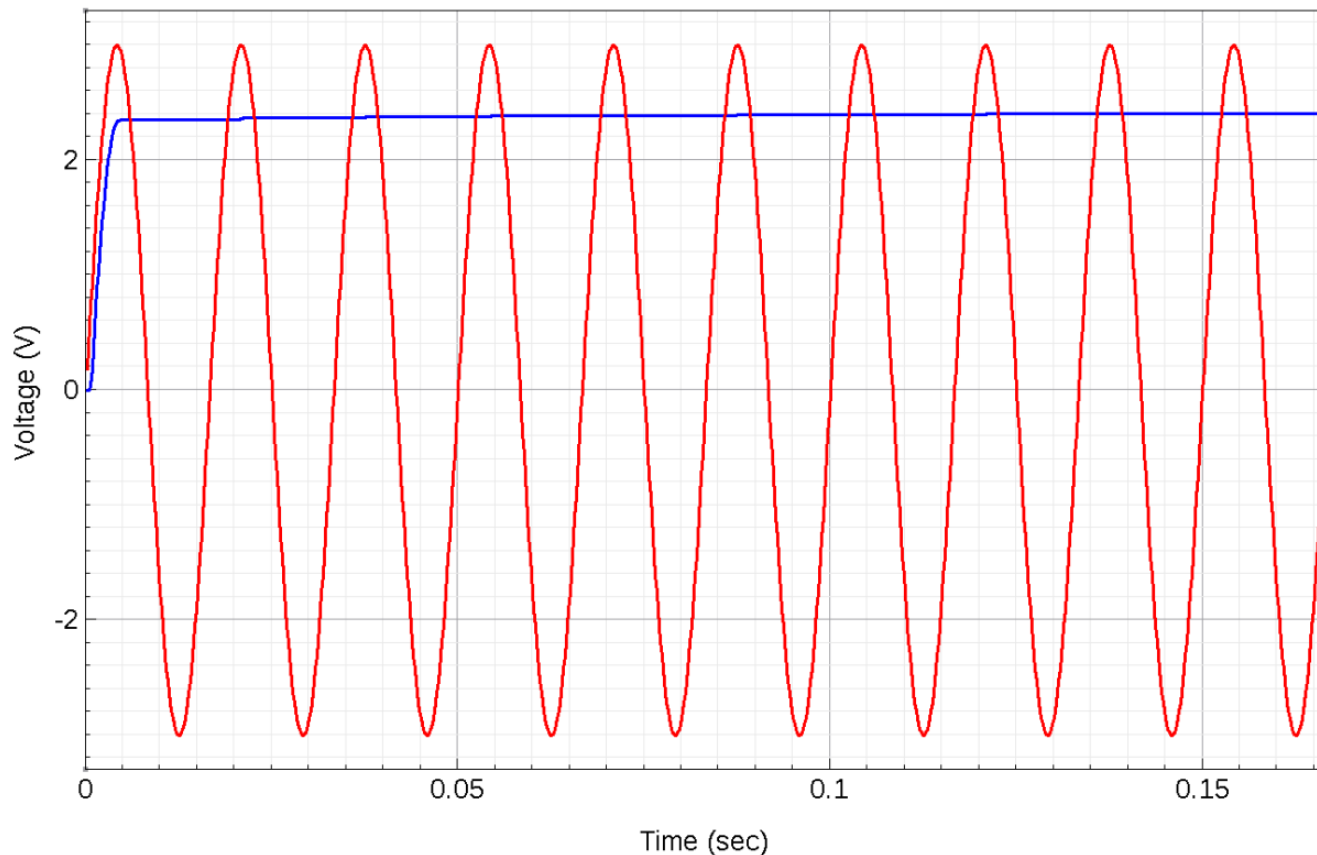
# Simulation result

---

- The capacitance,  $C_1 = 1 \mu\text{F}$ .
  - Generating a DC output





# Simple math

---

- Taylor series expansion
  - Consider a function,  $f(x)$ .
  - Then, at  $x_0 + \Delta x$  ( $\Delta x$  is small.), the function value would be similar to that at  $x_0$ :

$$f(x_0 + \Delta x) \approx f(x_0)$$

- A better approximation?

$$f(x_0 + \Delta x) \approx f(x_0) + \left. \frac{df(x)}{dx} \right|_{x=x_0} \Delta x$$

- Nonlinear function → linearly approximated!


# Nonlinear system

- A diode: Input  $V_D (= V_{anode} - V_{cathode})$ , output  $I_D (= I_{anode})$

$$V_D \rightarrow \boxed{I_D = I_S \exp \frac{V_D}{V_T}} \rightarrow I_D$$


- When  $V_{in} = 0.6 + 0.3 \sin 2\pi f t$ ,

Input voltage (V)

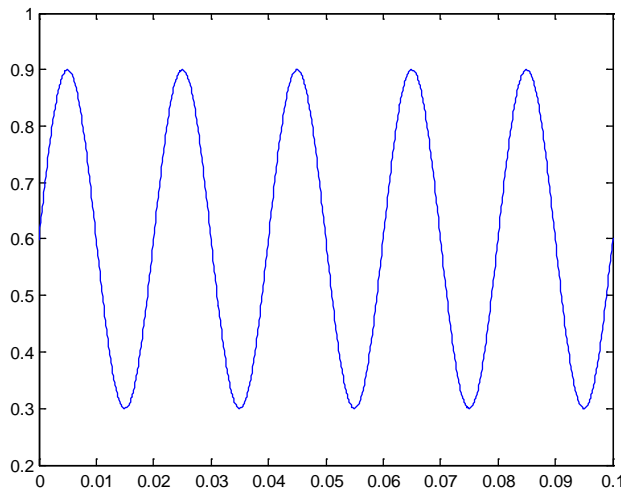

Time (sec)

Output current (A)

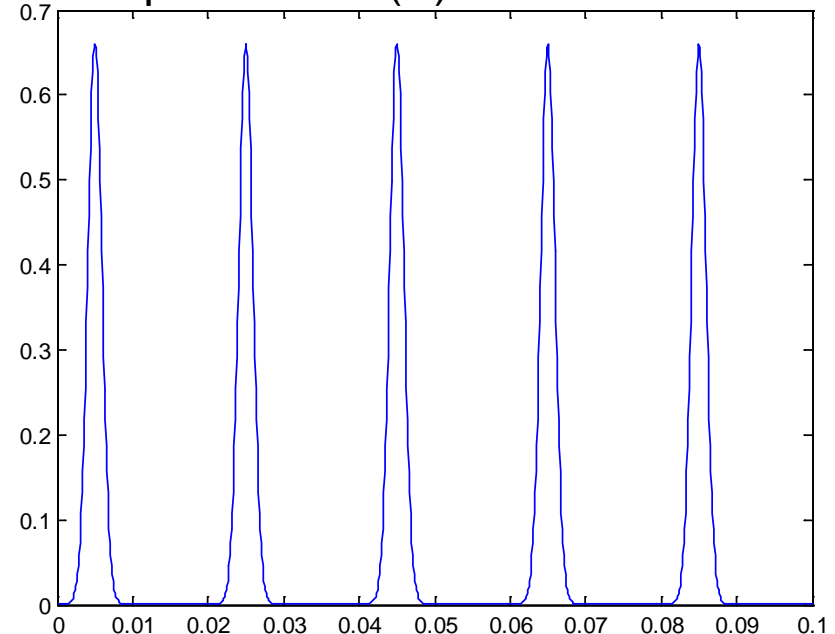


Time (sec)

# Small input amplitude

- When  $V_{in} = 0.6 + 0.001 \sin 2\pi f t$ ,
  - $I_D$  is almost sinusoidal.


Input voltage (V)

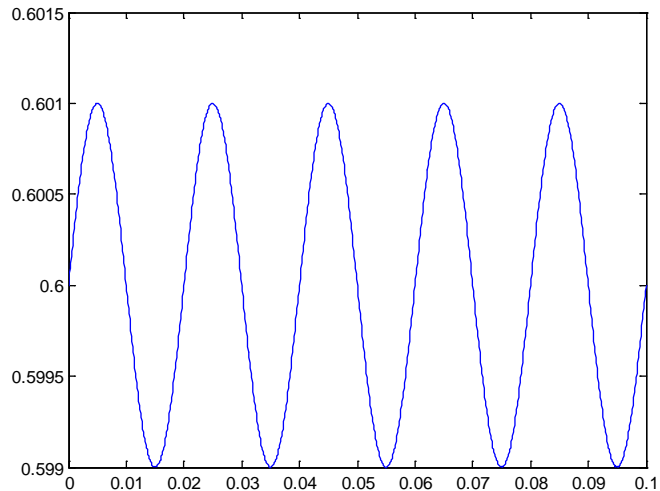

Time (sec)



Output current (A)


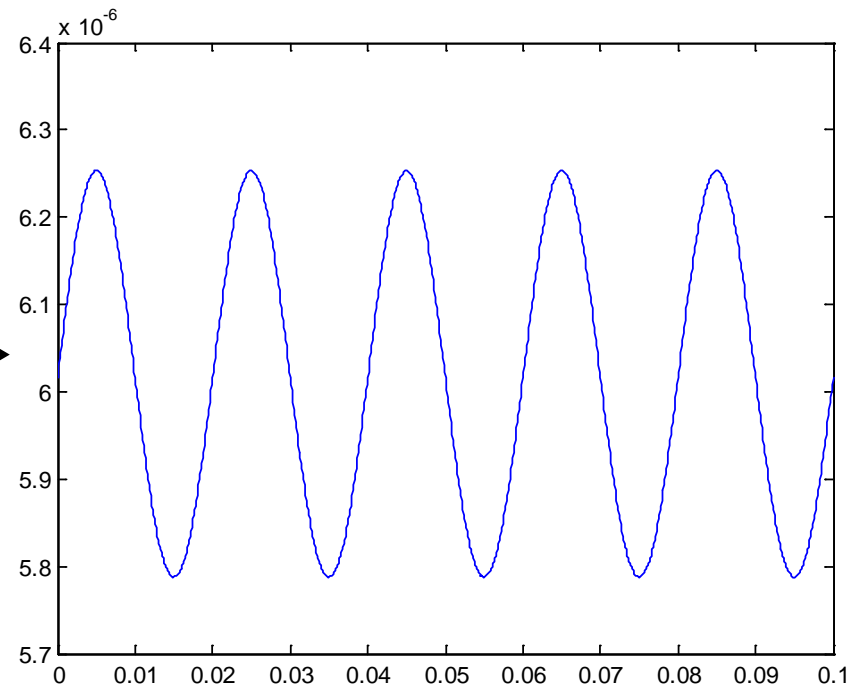


Time (sec)
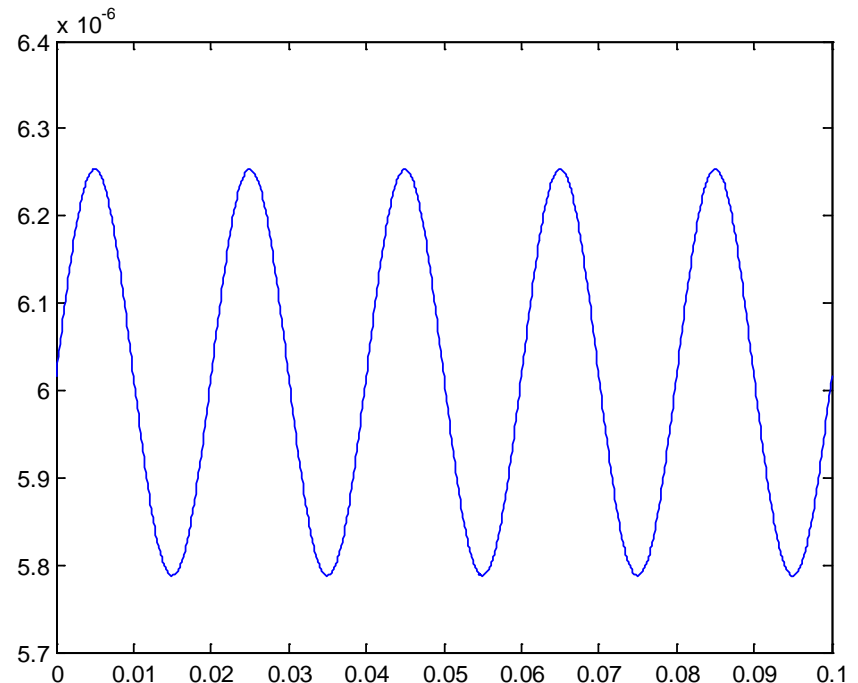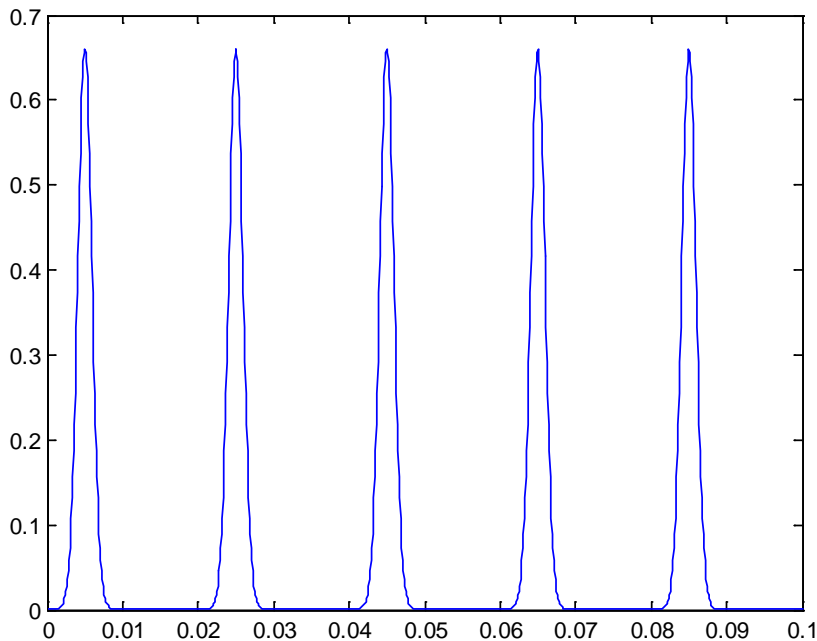
# Questions!

---

- You know the solution for  $V_{in} = 0.6 + \mathbf{0.3} \sin 2\pi ft$ .
  - Draw  $I_D(t)$  when  $V_{in} = 0.6 + \mathbf{0.6} \sin 2\pi ft$ .
- You know the solution for  $V_{in} = 0.6 + \mathbf{0.001} \sin 2\pi ft$ .
  - Draw  $I_D(t)$  when  $V_{in} = 0.6 + \mathbf{0.002} \sin 2\pi ft$ .



# Small-signal analysis

---

- General case

$$V_{D,DC} + v_{D,AC}(t) \rightarrow \boxed{I_D = I_S \exp \frac{V_D}{V_T}} \rightarrow I_{D,DC} + i_{D,AC}(t)$$

- “Small-signal” case

– When  $v_{D,AC}(t)$  is small, then, the AC current is given by

$$i_{D,AC}(t) \approx I_{D,DC} \frac{v_{D,AC}(t)}{V_T}$$

$$v_{D,AC}(t) \rightarrow \boxed{I_{D,AC}(t) = I_{D,DC} \frac{v_{D,AC}(t)}{V_T}} \rightarrow i_{D,AC}(t)$$

# Application to a diode

---

- Small-signal resistance

- As far as small changes in the diode current and voltage are concerned, the device behaves as a linear resistor.

$$r_d = \frac{V_T}{I_D}$$

- When the small change in the diode voltage is time-varying,

$$I_D(t) = I_s \exp \frac{V_{D,DC} + \Delta V \cos \omega t}{V_T} = I_s \exp \frac{V_{D,DC}}{V_T} \exp \frac{\Delta V \cos \omega t}{V_T}$$

$$I_D(t) \approx I_{D,DC} \left( 1 + \frac{\Delta V \cos \omega t}{V_T} \right)$$

- The AC output current has the same frequency!

# Razavi, Example 3.18

---

- A diode is biased at a current of 1 mA.

- Small-signal resistance is given by

$$r_d = \frac{V_T}{I_D} = 25.85 \, \Omega$$

- When an AC voltage with 1 mV amplitude is applied, the amplitude of the AC current is

$$\frac{1 \, \text{mV}}{r_d} = 38.7 \, \mu\text{A}$$

- A diode is biased at a current of 1  $\mu\text{A}$ .

- Small-signal resistance is given by

$$r_d = \frac{V_T}{I_D} = 25.85 \, \text{k}\Omega$$